

# **Transistor Sizing and Technology Scaling**

# **Transistor Sizing**

## **or**


### **T – Sizing**

# Noise Margin

- **Noise margin**

- is the amount of noise that a CMOS circuit could withstand without compromising the operation of circuit
- does make sure that any signal which is logic '1' with finite noise added to it, is still recognized as logic '1' & not logic '0'
- is a parameter closely related to the input-output voltage characteristics
- allows us to determine the allowable noise voltage on the input of a gate so that the output will not be affected

# Noise Margin

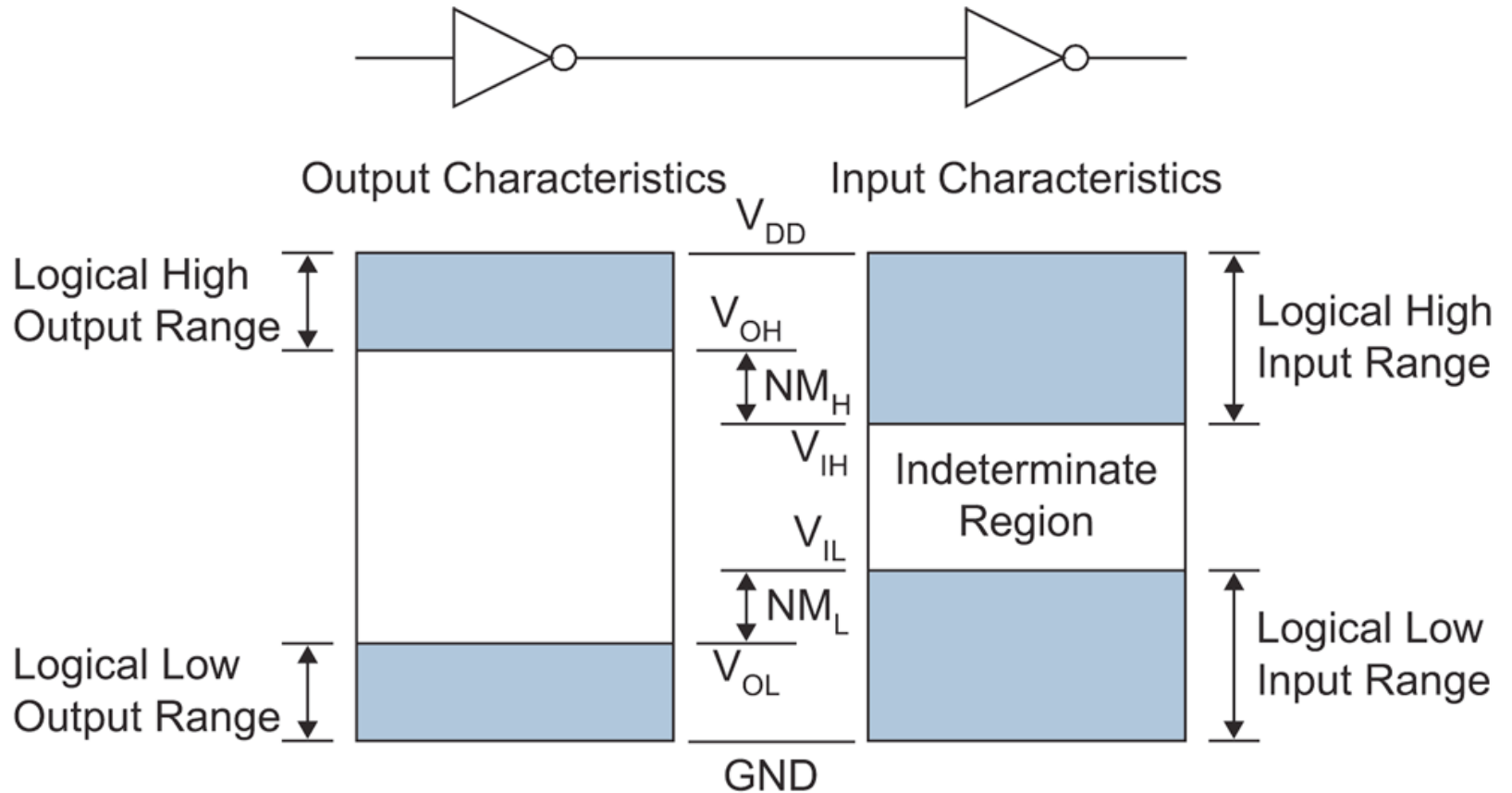

# Noise Margin

- Noise margin is specified in terms of 2 parameters:
  - LOW Noise Margin,  $\text{NM}_L$
  - HIGH Noise Margin,  $\text{NM}_H$


$$\text{NM}_L = |V_{\text{ILmax}} - V_{\text{OLmax}}|$$

$$\text{NM}_H = |V_{\text{OHmin}} - V_{\text{IHmin}}|$$


To optimize both noise margins  $\text{NM}_L$  and  $\text{NM}_H$  generally it is desirable to have  $V_{\text{IH}} = V_{\text{IL}}$  & this to be a value that is midway in the logic swing, that is  $V_{\text{DD}}/2$ .

$$\text{Or, } V_{\text{inv,th}} = V_{\text{DD}}/2$$

# Noise Margin

 

# The Ideal Gate

 

$$R_{in} = \infty$$

$$R_{out} = 0$$

$$\text{Noise Margin} = V_{DD}/2$$

$$\text{Gain} = \infty$$


- We know that, for a CMOS inverter:

$$V_{inv} = \frac{V_{DD} + V_{tp} + V_{tn} \sqrt{\frac{\beta_n}{\beta_p}}}{1 + \sqrt{\frac{\beta_n}{\beta_p}}}$$

- To make  $V_{th,inv} = V_{DD}/2$ ,  $\beta_n = \beta_p \rightarrow \mu_n C_{ox} W_n/L_n = \mu_p C_{ox} W_p/L_p$
- But  $\mu_n = 2.7\mu_p$
- Therefore,  **$W_p = 2.7W_n$**
- That is, PMOS is made 2.7 times wider than NMOS.





 - This trick of making the PMOS larger to compensate for the lower hole mobility is universally used in silicon design.
- However, making the PMOS 2.7 times larger than the NMOS leads to large circuits that occupy large areas of silicon for little extra benefit.



- If we examine Fig. above for  $V_{DD} = 5V$ , we see that the rate of change of  $V_{th,inv}$  w.r.t.  $W_p/W_n$  is large for  $W_p/W_n < 1$ , but is smaller for  $W_p/W_n > 1$ . Because of the diminishing improvement in  $V_{th,inv}$  for increasing  $W_p/W_n$  there is little reward for making  $W_p/W_n$  large. In practice, real designs use a compromise value for  $W_p/W_n$  – typically in the range 1.5 to 2.0
- The adroit selection of transistor dimensions is known as **T-sizing**.

# T – Sizing Standard Gates

  

- In NAND gate above, there are two parallel PMOSs between  $V_{DD}$  and Z. If one PMOS is OFF and the other is ON, then the pull-up strength of the gate will be the same as that of an inverter with a similarly sized PMOS
- However, the NMOSs, both must be ON at once to pull down Z. There are two NMOSs, hence two ON resistances added in series between  $V_{SS}$  and Z. Hence, the pull-down strength of a NAND gate will be less than that of an inverter with a similarly sized NMOS. This problem is solved by T-sizing

# Stacks and Stack Depth

- The N-block and P-blocks of CMOS gates are often referred to as *stacks*
- Each gate can have one or more circuit paths connecting the o/p to one or other of the supply rails, & the number of transistors that appears in any path is referred to as the *stack depth*.

## *Examples:*

- The NAND gate has an N-stack depth of 2 and a P-stack depth of 1
- The NOR gate has an N-stack depth of 1 and a P-stack depth of 2

- If we want to make a NAND gate have the same transfer characteristic as an inverter with  $W_{ip}$  and  $W_{in}$ , then the MOSFETs in the NAND gate will have  $W_{np} = W_{ip}$  and  $W_{nn} = 2W_{in}$

$$W_{np} = S_p W_{ip} \quad \text{and} \quad W_{nn} = S_n W_{in}$$

- where  $S_p$  is the P-stack depth and  $S_n$  is the N-stack depth

# T – Sizing Compound Gates

- The method of T-sizing discussed so far is reliable and easy to apply for simple, single logic function gates, but is less straightforward to apply to compound gates.

*Example:*


$$Z = \overline{(A + B).C + D}$$

PMOS paths	NMOS paths	Stack depth ( $S$ )	New $W_p$	New $W_n$

# T – Sizing Compound Gates

- The method of T-sizing discussed so far is reliable and easy to use for simple, single logic function gates, but is less straightforward to apply to compound gates.

*Example:*

 

$$Z = \overline{(A.B + C).D}$$

# The Problem

PMOS paths	NMOS paths	Stack depth ( $S$ )	New $W_p$	New $W_n$
A-C	B-A-D C-D	2	$2W_{ip}$	$3W_{in}$ $2W_{in}$
B-C		2	$2W_{ip}$	
D		1	$W_{ip}$	
		3		
		2		


- This procedure generates an anomaly – NMOS **D** is required to have two different sizes. This is clearly impossible to achieve.




# The Solution

- A variety of solutions to this problem have been proposed, but the problem is not strictly tractable.

Here are a few:

 1. T-size the deepest stack first.
  2. T-size the least deep stack first
  3. Use sub-linear scaling – e.g. multiply by  $\sqrt{S}$  instead of  $S$
- 
- Linear Scaling



N- or PMOS (by input label)	Method 1 Linear – deepest stack first		Method 2 Linear – least deep stack first		Method 3 Sub-linear ( $\sqrt{\phantom{x}}$ ) – deepest stack first	
	New $W_p$	New $W_n$	New $W_p$	New $W_n$	New $W_p$	New $W_n$
A	$2W_{ip}$	$3W_{in}$	$2W_{ip}$	$4W_{in}$	$1.4W_{ip}$	$1.7W_{in}$
B	$2W_{ip}$	$3W_{in}$	$2W_{ip}$	$4W_{in}$	$1.4W_{ip}$	$1.7W_{in}$
C	$2W_{ip}$	$1.5W_{in}$	$2W_{ip}$	$2W_{in}$	$1.4W_{ip}$	$1.22W_{in}$
D	$W_{ip}$	$3W_{in}$	$W_{ip}$	$2W_{in}$	$W_{ip}$	$1.7W_{in}$

# Assignments

- Design gates with the following logic functions and T-size them using all linear and sub-linear methods:

$$Z = \overline{(A.B + C.D).E}$$

$$Z = \overline{(A + B).C + D}$$

# **Technology Scaling**

# Typical Scaling Scenario


- 1974: 5 $\mu$ m Technology,  $V_{DD} = 10V$
- 1984: 1 $\mu$ m Technology,  $V_{DD} = 5V$
- 1994: 0.35 $\mu$ m Technology,  $V_{DD} = 3.5V$
- 2004: 90nm Technology,  $V_{DD} = 1V$
- 2014: 15nm Technology,  $V_{DD} = 0.8V$
- 2018: 10nm Technology,  $V_{DD} = 0.5V$

# Technology Scaling

- Technology scaling has a threefold objective:
  - Increase the transistor density
  - Reduce the gate delay
  - Reduce the power consumption
- At present, between two technology generations, the objectives are:
  - Doubling of the transistor density
  - Reduction of the gate delay by 30% (at 43% increase in frequency)
  - Reduction of the power by 50% (at 43% increase in frequency)

# Technology Scaling

## Bulk nMOSFET

 

Device Parameter
Length, $L$
Width, $W$
Gate oxide thickness, $t_{ox}$
Supply voltage, $V_{DD}$
Threshold voltages, $V_{tn}$ , $V_{tp}$
Substrate doping, $N_A$

# Why odd numbers?

0.25μ, 0.18μ, 0.13μ, 90nm and 65nm technologies,  
continuing on to 15nm and 10nm, 7nm, 5nm



# Technology Scaling

- A scaling factor ( $S$ ) reduces device dimensions as  $1/S$ .
- Successive generations of technology have used a scaling  $S = \sqrt{2}$ , doubling the number of transistors per unit area. This produced  $0.25\mu$ ,  $0.18\mu$ ,  $0.13\mu$ ,  $90\text{nm}$  and  $65\text{nm}$  technologies, continuing on to  $7\text{nm}$  and  $5\text{nm}$  ...
- A 5% gate shrink ( $S = 1.05$ ) is commonly applied to boost speed as the process matures.

N. H. E. Weste and D. Harris, *CMOS VLSI Design, Third Edition*, Boston: Pearson Addison-Wesley, 2005, Section 4.9.1.

# Technology Scaling

1. Constant Field Scaling
2. Constant Voltage Scaling
3. Lateral Scaling

# Constant Electric Field Scaling

Device Parameter	Scaling
Length, $L$	$1/S$
Width, $W$	$1/S$
Gate oxide thickness, $t_{ox}$	$1/S$
Supply voltage, $V_{DD}$	$1/S$
Threshold voltages, $V_{tn}$ , $V_{tp}$	$1/S$
Substrate doping, $N_A$	$S$

# Constant Electric Field Scaling (Cont.)

Device Characteristic		Scaling
$\beta$	$W / (L t_{ox})$	$S$
Current, $I_{ds}$	$\beta (V_{DD} - V_t)^2$	$1/S$
Resistance, $R$	$V_{DD} / I_{ds}$	$1$
Gate capacitance, $C$	$W L / t_{ox}$	$1/S$
Gate delay, $\tau$	$RC$	$1/S$
Clock frequency, $f$	$1/\tau$	$S$
Dynamic power per gate, $P$	$CV^2 f$	$1/S^2$
Chip area, $A$		$1/S^2$
Power density	$P/A$	$1$
Current density	$I_{ds}/A$	$S$

**Table 4.12** Influence of scaling on MOS device characteristics

Parameter	Sensitivity	Constant Field	Lateral	Constant Voltage
Scaling Parameters				
Length: $L$		$1/S$	$1/S$	$1/S$
Width: $W$		$1/S$	1	$1/S$
Gate oxide thickness: $t_{ox}$		$1/S$	1	$1/S$
Supply voltage: $V_{DD}$		$1/S$	1	1
Threshold voltage: $V_{tm}, V_{tp}$		$1/S$	1	$1/S$
Substrate doping: $N_A$		$S$	1	$S$
Device Characteristics				
$\beta$	$\frac{W}{L} \frac{1}{t_{ox}}$	$S$	$S$	$S$
Current: $I_{ds}$	$\beta(V_{DD} - V_t)^2$	$1/S$	$S$	$1/S$
Resistance: $R$	$\frac{V_{DD}}{I_{ds}}$	1	$1/S$	1
Gate capacitance: $C$	$\frac{WL}{t_{ox}}$	$1/S$	$1/S$	$1/S$
Gate delay: $\tau$	$RC$	$1/S$	$1/S^2$	$1/S$
Clock frequency: $f$	$1/\tau$	$S$	$S^2$	$S$
Dynamic power dissipation (per gate): $P$	$CV^2f$	$1/S^2$	$S$	$1/S$
Chip area: $A$		$1/S^2$	1	$1/S^2$
Power density	$P/A$	1	$S$	1
Current density	$I_{ds}/A$	$S$	$S$	$S$