 



Power Dissipation in CMOS

Single Channel Inverters




NELS

$$P \propto V_{DD}^3$$

 


NELT

$$P \propto V_{DD}^3$$

 

HMOS


$$P \propto V_{DD}$$

 

Pseudo-nMOS

$$P \propto V_{DD}^3$$

CMOS Logic (Inverter)

 

No static leakage path exists for either 1 or 0 input.

Components of Power Dissipation

□ Dynamic Component (P_{dyn})

■ Switching p.d. (P_{sw})

- Logic activity
- Glitches

■ Short-circuit p.d. (P_{sc})

□ Static Component (P_{stat})


■ Leakage p.d.


$$\begin{aligned} P_{total} &= P_{dyn} + P_{stat} \\ &= (P_{sw} + P_{sc}) + P_{stat} \end{aligned}$$

$$I_D = I_S \left(e^{\frac{V_{DQ}}{kT}} - 1 \right)$$


For a small-geometry IC diode, $I_S = 1E^{-16}$.

Switching Power : P_{SW}

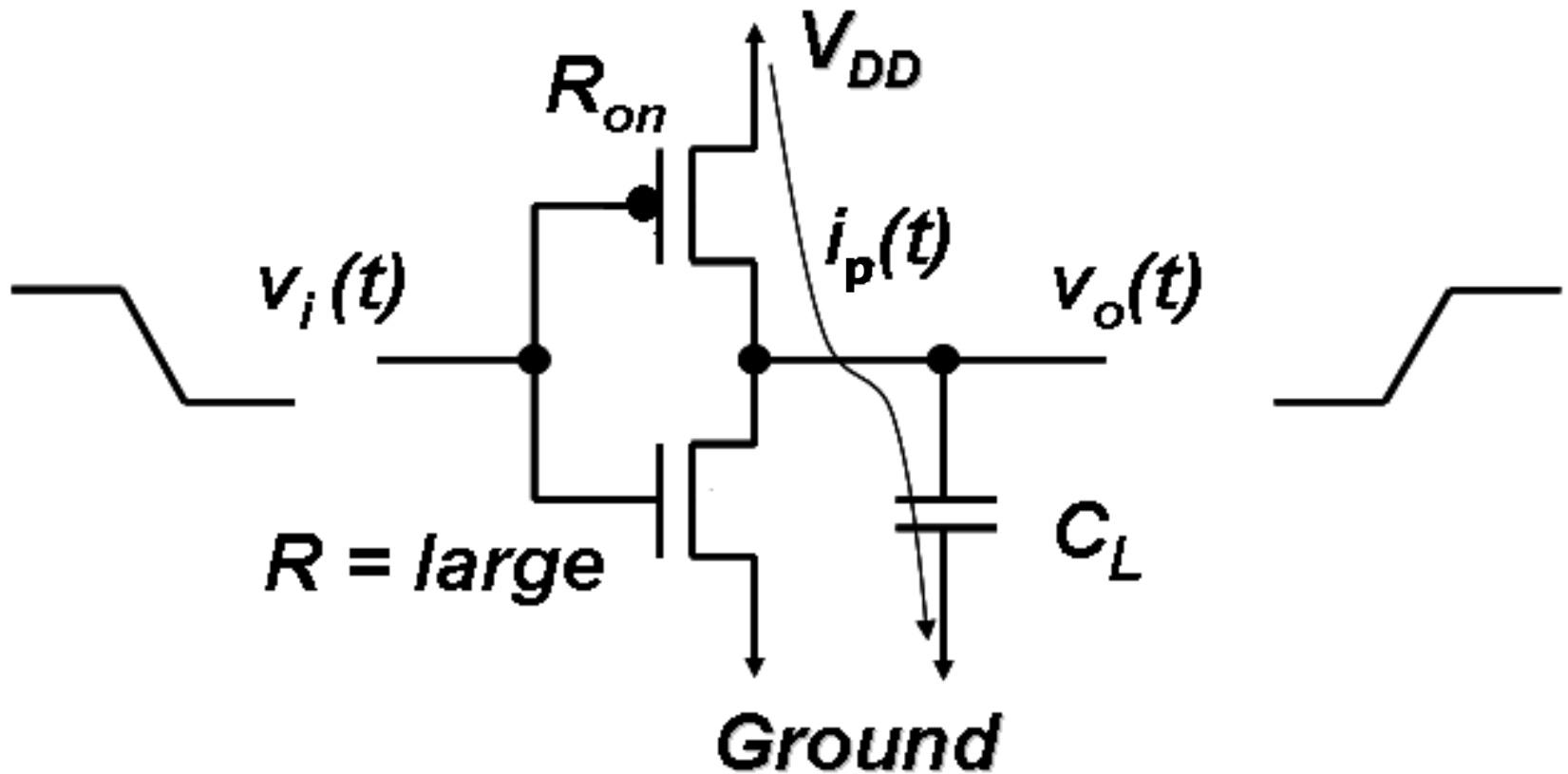

 

$$P = V \times I$$

 


Switching Power : P_{sw}

$$P_{sw} = \frac{1}{T} \int_0^{T/2} i_N(t) V_{Out} dt + \frac{1}{T} \int_{T/2}^T i_P(t) (V_{DD} - V_{Out}) dt$$

Since $i_N(t) = C_L dV_{Out}/dt$ and analogously for $i_P(t)$,

$$P_{sw} = \frac{C_L}{T} \int_0^{V_{DD}} V_{Out} dV_{Out} + \frac{C_L}{T} \int_{V_{DD}}^0 (V_{DD} - V_{Out}) d(V_{DD} - V_{Out})$$

$$P_{sw} = \frac{C_L V_{DD}^2}{T}$$

 

Switching Power : P_{sw}

- Gate output rising transition
 - Energy stored in capacitor = $C_L V_{DD}^2 / 2$
 - Energy dissipated in pMOS transistor = $C_L V_{DD}^2 / 2$
- Gate output falling transition
 - Energy dissipated in nMOS transistor = $C_L V_{DD}^2 / 2$
- Energy dissipated per transition = $C_L V_{DD}^2$

∴ Total Power dissipation:

$$P_{sw} = C_L V_{DD}^2 / T$$

Lowering Switching Power:

Capacitance:

Function of Fan-out, Wire length and transistor sizes.

Clock Frequency:

Increasing

$$P_{sw} = C_L V_{DD}^2 f_{CLK} \alpha$$

Supply voltage:


Dropping with Successive generations

Activity factor:

How often, on average, do a node switch?

Activity factor

$$P_{sw} = C_L V_{DD}^2 f_{CLK} \alpha$$

 


$$P_{sw} = C_L V_{DD}^2 f_{CLK} \alpha$$

- Even though power dissipation takes place in a channel resistance, in the equation above the resistance parameter is missing and the power is independent of resistance. Why?

Glitches

 - ❑ Glitches are temporary changes in the value of the output – unnecessary transitions.
- ❑ Are caused due to the skew in the input signals to a gate.



Type of Logic Function: NOR vs. XOR

Example: Static 2-input NOR Gate

<i>A</i>	<i>B</i>	<i>Out</i>
0	0	1
0	1	0
1	0	0
1	1	0

Assume signal probabilities

$$p_{A=1} = 1/2$$

$$p_{B=1} = 1/2$$

Then transition probability

$$p_{0 \rightarrow 1} = p_{Out=0} \times p_{Out=1}$$

$$= 3/4 \times 1/4 = 3/16$$

If inputs switch every cycle

$$\alpha_{0 \rightarrow 1} = 3/16$$

Type of Logic Function: NOR vs. XOR

Example: Static 2-input XOR Gate

<i>A</i>	<i>B</i>	<i>Out</i>
0	0	0
0	1	1
1	0	1
1	1	0

Assume signal probabilities

$$p_{A=1} = 1/2$$

$$p_{B=1} = 1/2$$

Then transition probability


$$p_{0 \rightarrow 1} = p_{Out=0} \times p_{Out=1}$$

$$= 1/2 \times 1/2 = 1/4$$


If inputs switch in every cycle

$$\alpha_{0 \rightarrow 1} = 1/4$$

Dynamic Gate

 

CLK Waveform

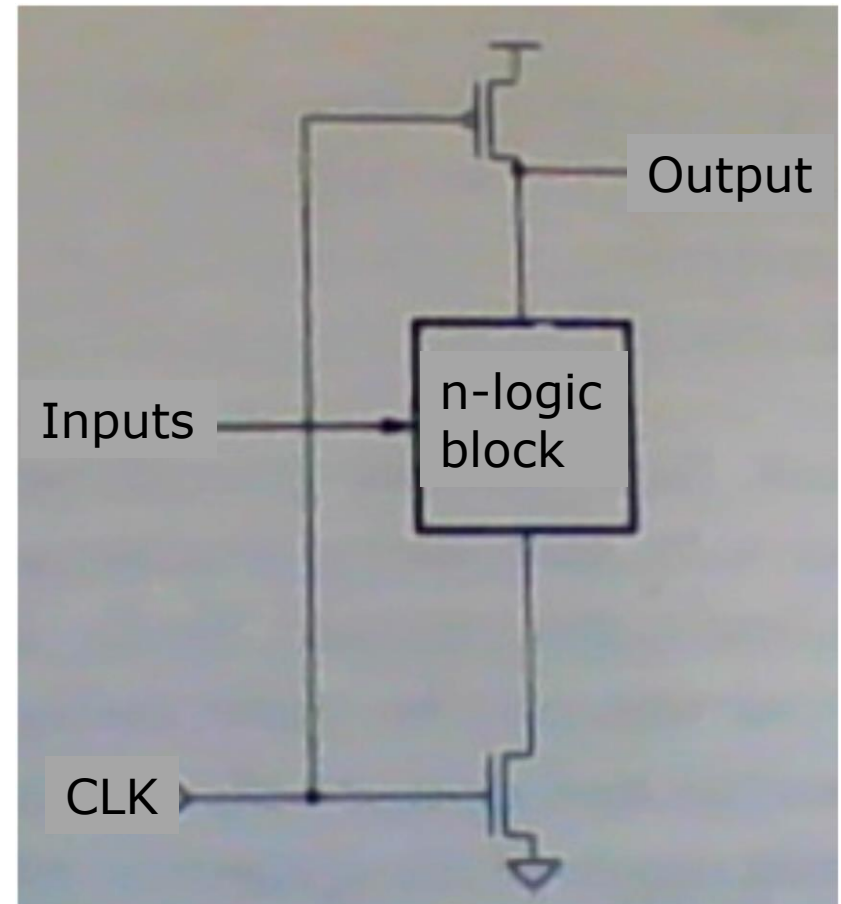

Dynamic Power Consumption is Data Dependent

Dynamic 2-input NOR Gate

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

Assume signal probabilities

$$P_{A=1} = 1/2$$

$$P_{B=1} = 1/2$$

Then transition probability

$$P_{0 \rightarrow 1} = P_{\text{out}=0} \times P_{\text{out}=1}$$

$$= 3/4 \times 1 = 3/4$$

Switching activity always higher in dynamic gates!

$$P_{0 \rightarrow 1} = P_{\text{out}=0}$$

Glitch Power Dissipation

- Depending on the skew, the gate output voltage may perform a full swing or not.
- An approximation of the energy drawn during the glitch is:

$$P_{glitch} = \frac{1}{T} \cdot C_{load} \cdot V_{dd} \cdot \sum_{i=1}^n \Delta V_n$$

Where ΔV_n is the voltage swing of a sequence of n incomplete transitions within a period of T .

Components of Power Dissipation

□ Dynamic Component (P_{dyn})

■ Switching p.d. (P_{sw})

- Logic activity
- Glitches


■ Short-circuit p.d. (P_{sc})


□ Static Component (P_{stat})


■ Leakage p.d.

$$\begin{aligned} P_{total} &= P_{dyn} + P_{stat} \\ &= (P_{sw} + P_{sc}) + P_{stat} \end{aligned}$$

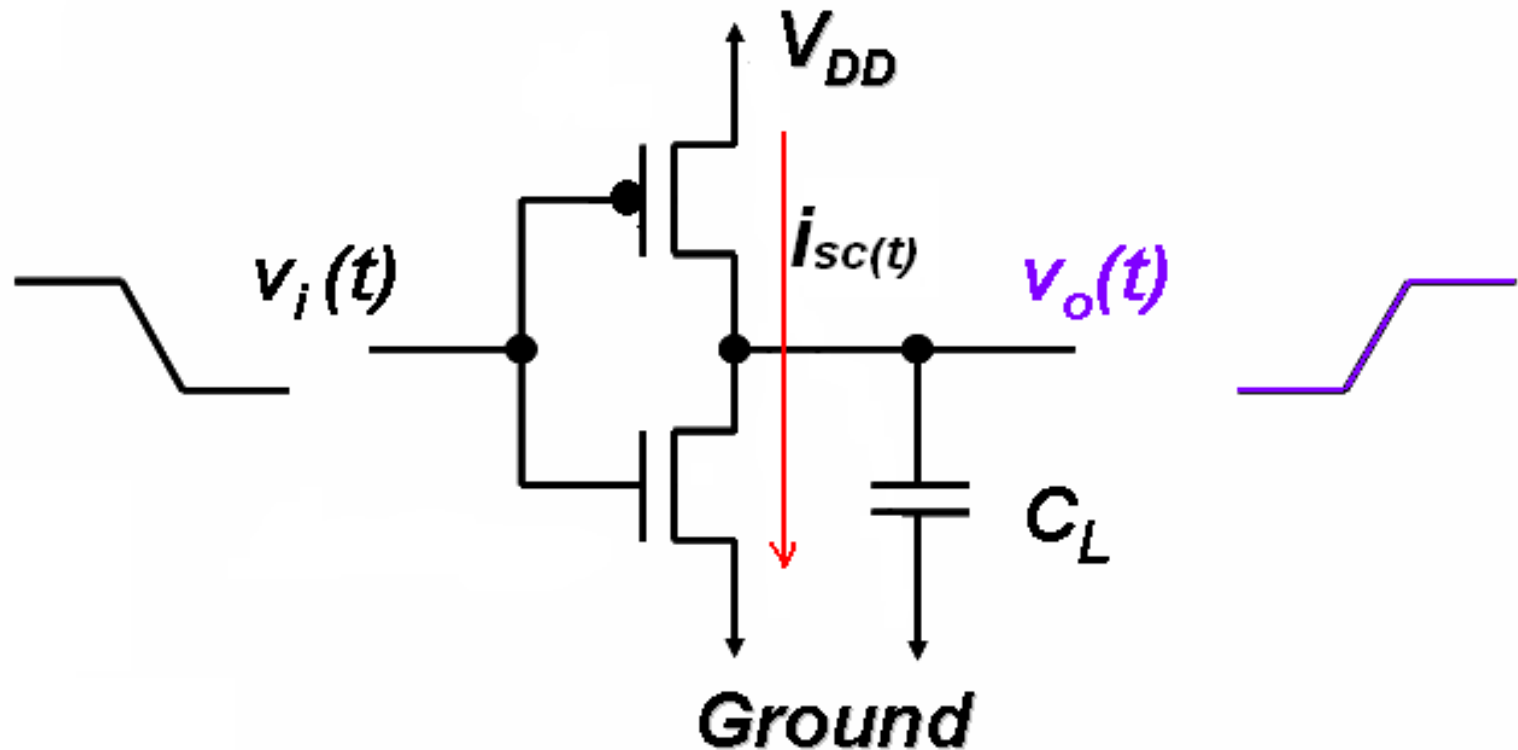Short Circuit Power of a Transition: P_{sc}



 

 

The short-circuit power dissipation is given by

$$P_{sc} = I_{mean} \cdot V_{DD}$$

For the input waveform shown, which depicts the short circuit in an unloaded inverter,

$$I_{mean} = 2 \times \left[\frac{1}{T} \int_{t_1}^{t_2} I(t) dt + \frac{1}{T} \int_{t_2}^{t_3} I(t) dt \right]$$

assuming that $V_{tn} = -V_{tp}$ and $\beta_n = \beta_p (= \beta)$ and that the behavior is symmetrical around t_2 .

$$= 2 \times \frac{2}{T} \int_{t_1}^{t_2} \frac{\beta}{2} (V_{in}(t) - V_t)^2 dt$$

with

$$V_{in}(t) = \frac{V_{DD}}{t_r} t ; \quad t_1 = \frac{V_{tn}}{V_{DD}} t_r ; \quad t_2 = \frac{t_r}{2}$$

Peak Short Circuit Current

For an unloaded inverter, assuming that $t_r = t_f = \tau$

$$P_{SC} = \frac{\beta}{12} (V_{DD} - V_{TH})^3 \frac{\tau}{T}$$

- ❑ Increases with the size (or gain, β) of transistors
- ❑ Increases with rise and fall times of input
- ❑ Decreases and eventually becomes zero when V_{DD} is scaled down but the threshold voltages are not scaled down.
- ❑ Decreases with load capacitance, C_L
- ❑ Largest when $C_L = 0$

Summary: Short-Circuit Power

- ❑ Short-circuit power is consumed by each transition (increases with input transition time).
- ❑ Reduction requires that gate output transition should not be faster than the input transition (faster gates can consume more short-circuit power).
- ❑ Scaling down of supply voltage with respect to threshold voltages reduces short-circuit power; completely eliminated when $V_{DD} \leq |V_{tp}| + V_{tn}$.

Solution:

- Theorem – A CMOS gate consumes no short-circuit power when $V_{DD} \leq V_{tn} + |V_{tp}|$, i.e., supply voltage is lower than the sum of the threshold voltage magnitudes for the n and p channel MOSFETs.
- Proof: The short-circuit conduction requires that a pull-up path through pMOS devices and a pull-down path through nMOS devices should be simultaneously on. If the common gate voltage for both devices is V_{in} , where $0 \leq V_{in} \leq V_{DD}$, then a necessary condition for short-circuit conduction is:

$$V_{tn} \leq V_{in} \leq V_{DD} - |V_{tp}|$$

In order to make this condition impossible, we must ensure that the upper bound on V_{in} does not exceed the lower bound. Thus,


$$V_{DD} - |V_{tp}| \leq V_{tn}$$

Therefore, $V_{DD} \leq V_{tn} + |V_{tp}|$

Components of Power


- Dynamic
 - Signal transitions
 - Logic activity
 - Glitches
 - Short-circuit
- Static
 - Leakage

Leakage Power:

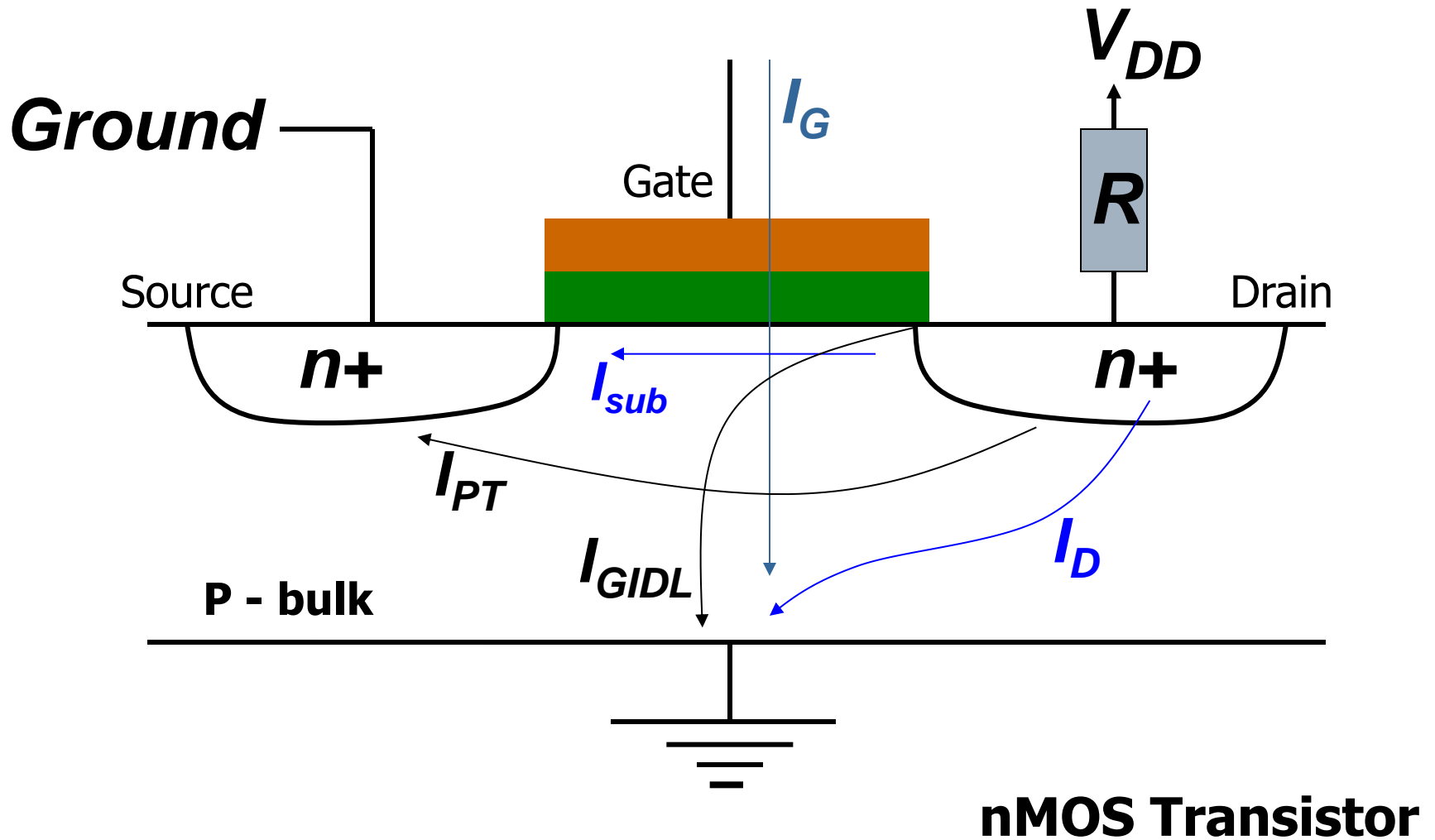

Leakage Current Components

 1. Subthreshold leakage, I_{sub}
2. Reverse bias pn junction leakage, I_D
3. Gate induced drain leakage, I_{GIDL} due to tunneling at the gate-drain overlap
4. Drain source punch-through, I_{PT} due to short channel and high drain-source voltage
5. Gate tunneling, I_G through thin oxide; *may become significant with scaling.*



1. Subthreshold Leakage, I_{sub}

- Occurs when $V_{GS} < V_{TH}$ (weak inversion), where minority carrier concentration is small, but not zero.
- Subthreshold conduction is dominated by the diffusion current
- This leakage component is the dominant modern device OFF-state leakage due to the low V_{TH} that is used.

Subthreshold Leakage, I_{sub}

a) For Long Channel Devices:

$$I_{sub} = \mu_0 C_{ox} (W/L) v_T^2 \exp \{ (V_{GS} - V_{TH}) / \eta v_T \}$$

μ_0 : zero bias carrier surface mobility

C_{ox} : gate oxide capacitance per unit area

L : channel length


W : gate width

$v_T = kT/q$: thermal voltage

η : a technology parameter

Where, $\eta = 1 + \frac{C_b}{C_g}.$
 
$$C_b = \frac{\epsilon_{si}}{w_d}, \quad C_g = \frac{\epsilon_{ox}}{t_{ox}}.$$



where ϵ_{ox} and ϵ_{si} denote the dielectric constants of the oxide and silicon, resp, w_d is the depletion width under the *channel* and t_{ox} is the gate oxide thickness.

b) For Short Channel Devices:

$$I_{sub} = \mu_0 C_{ox} (W/L) v_T^2 \exp\{(V_{GS} - V_{TH} + nV_{DS})/\eta v_T\}$$

V_{DS} = drain to source voltage
 n : a DIBL constant

W. Nebel and J. Mermet (Editors), *Low Power Design in Deep Submicron Electronics*, Springer, 1997, Section 4.1 by J. Figueras, pp. 81-104