



# **CMOS Switching Characteristics**

# CMOS Switching Characteristics

- To describe the switching characteristics of a CMOS inverter we develop 2 models:
  1. Analytic Delay Model
  2. Empirical Delay Model
- These models help to understand the parameters that affect CMOS delay
- The switching speed of a CMOS gate is limited by the time taken to charge and discharge the load capacitance  $C_L$
- An input transition results in an output transition that either charges  $C_L$  toward  $V_{DD}$  or discharge  $C_L$  toward  $V_{SS}$

 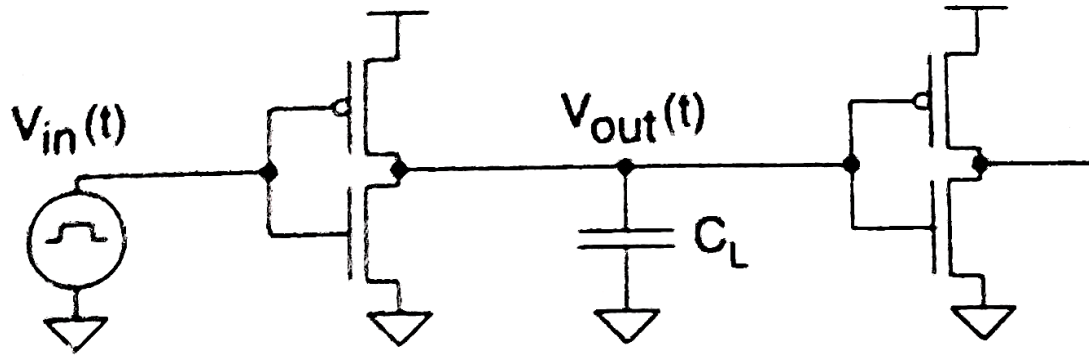
# Delay – Definitions

- **Rise time**,  $t_r$  = time for a waveform to rise from 10% to 90% of its steady-state value
- **Fall time**,  $t_f$  = time for a waveform to fall from 90% to 10% of its steady-state value
- **Delay time**,  $t_d$  = time difference between input transition (50%) and the 50% output level. (This is the time taken for a logic transition to pass from input to output)



Switching characteristic for CMOS inverter

# Analytic Delay Model

 





Trajectory of n-transistor operating point during Switching when the input  $V_{in}(t)$  is a step wave form

# Analytic Delay Model

## Fall Time:

The fall time,  $t_f$ , consists of 2 intervals:

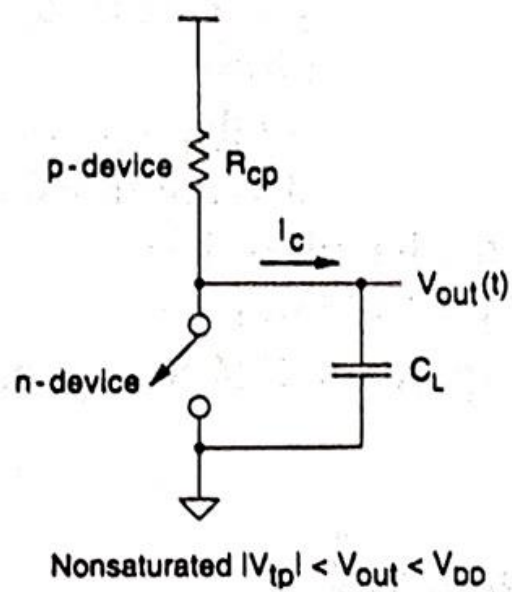   1.  $t_{f1}$  = period during which the capacitor voltage,  $V_{out}$ , drops from  $0.9V_{DD}$  to  $(V_{DD} - V_{tn})$
2.  $t_{f2}$  = period during which the capacitor voltage,  $V_{out}$ , drops from  $(V_{DD} - V_{tn})$  to  $0.1V_{DD}$



When the n-device is operating in the saturation region,

$$C_L \frac{dV_{out}}{dt} + \frac{\beta_n}{2} (V_{DD} - V_{tn})^2 = 0.$$

Integrating from  $t = t_1$ , corresponding to  $V_{out} = 0.9 V_{DD}$ , to  $t = t_2$  corresponding to  $V_{out} = (V_{DD} - V_{tn})$  results in

$$\begin{aligned} t_{f1} &= 2 \frac{C_L}{\beta_n (V_{DD} - V_{tn})^2} \int_{V_{DD} - V_{tn}}^{0.9 V_{DD}} dV_{out} \\ &= \frac{2 C_L (V_{tn} - 0.1 V_{DD})}{\beta_n (V_{DD} - V_{tn})^2} \end{aligned}$$



When the n-device begins to operate in the linear region, the discharge current is no longer constant. The  $t_{f2}$  taken to discharge the capacitor from  $(V_{DD}-V_{tn})$  to  $0.1V_{DD}$  can be obtained as,

$$\begin{aligned}
 t_{f2} &= \frac{C_L}{\beta_n (V_{DD} - V_{tn})} \int_{0.1 V_{DD}}^{V_{DD} - V_{tn}} \frac{dV_{out}}{\frac{V_{out}^2}{2(V_{DD} - V_{tn})} - V_{out}} \\
 &= \frac{C_L}{\beta_n (V_{DD} - V_{tn})} \ln \left( \frac{19V_{DD} - 20V_{tn}}{V_{DD}} \right) \\
 &= \frac{C_L}{\beta_n V_{DD} (1 - n)} \ln (19 - 20n),
 \end{aligned}$$

with  $n = V_{tn}/V_{DD}$ .

Thus the complete term for the fall time,  $t_f$  is

$$t_f = 2 \frac{C_L}{\beta_n V_{DD} (1 - n)} \left[ \frac{(n - 0.1)}{(1 - n)} + \frac{1}{2} \ln (19 - 20n) \right]$$

- The fall time,  $t_f$ , can be approximated as,

$$t_f = k \times \frac{C_L}{\beta_n V_{DD}}$$

- This implies the delay is directly proportional to the load capacitance. Hence, to achieve high speed circuits  $C_L$  must be minimized
- Secondly, it is inversely proportional to supply voltage. That is, as the supply voltage is raised the delay time is reduced
- Finally, the delay is inversely proportional to the  $\beta$  of the driving transistor and hence the delay decreases with  $\beta$

## Rise Time:

- Due to the symmetry of the CMOS circuit, a similar approach may be used to obtain the rise time,  $t_r$

$$t_r = 2 \frac{C_L}{\beta_p V_{DD} (1-p)} \left[ \frac{(p-0.1)}{(1-p)} + \frac{1}{2} \ln(19-20p) \right]$$

with  $p = |V_{tp}|/V_{DD}$ .

As before, this may be approximated by

$$t_r \cong 3 \rightarrow 4 \frac{C_L}{\beta_p V_{DD}}.$$

For equally sized n- and p-transistors, where  $\beta_n = 2\beta_p$ ,

$$t_f = \frac{t_r}{2}.$$

- Thus the fall time is faster than the rise time.
- Therefore, if we want to have approximately the same rise and fall time for an inverter, we need to make,

$$\beta_n / \beta_p = 1$$

- This implies that the channel width for the p-device must be increased to approximately 2 to 3 times that of the n-device, so

$$w_p = 2 - 3w_n$$

## Delay Time:

- In most CMOS circuits, the delay of a single gate is dominated by the output rise and fall times. The delay is approximately given by

$$t_{dr} = \frac{t_r}{2} \quad \text{and} \quad t_{df} = \frac{t_f}{2}$$

An alternative formulation is given by

$$t_{df} = A_N \frac{C_L}{\beta_n},$$

where  $A_N$  is a process constant for a specific supply voltage.  
 $A_N$  has been derived as

$$A_N = \frac{1}{V_{DD}(1-n)} \left[ \frac{2n}{1-n} + \ln \left( \frac{2(1-n) - V_O}{V_O} \right) \right],$$

where

$$n = \frac{V_{in}}{V_{DD}} \quad \text{and} \quad V_O = \frac{V_{out}}{V_{DD}}$$

For  $V_{tn} = 0.7$  volts,  $V_{DD} = 5$  volts,  $V_{out} = 2.5$  volts,  $A_N$  is .283.  
Similarly,

$$t_{dr} = A_p \frac{C_L}{\beta_p},$$

where  $A_p$  is a process constant for a specific supply voltage.  
 $A_p$  has been derived as

$$A_p = \frac{1}{V_{DD}(1+p)} \left[ \frac{-2p}{1+p} + \ln \left( \frac{2(1+p) - V_O}{V_O} \right) \right],$$

where

$$p = \frac{V_{tp}}{V_{DD}}$$

For  $V_{tp} = -0.7$ ,  $V_{DD} = 5$ ,  $V_{out} = 2.5$ ,  $A_p$  is .283.

The average gate delay for rising and falling transitions is

$$t_{av} = \frac{t_{df} + t_{dr}}{2}.$$

- Fig. below illustrates a SPICE simulation of a step input applied to an inverter driving a capacitive load.
- The process parameters for the simulation are:

$$V_{tn} = 0.767 \text{ volts}, V_{tp} = -0.938 \text{ volts}, \beta_n = 4.04 \times 10^{-4}, \beta_p = 3.48 \times 10^{-4}, \\ V_{DD} = 5 \text{ volts}, C_L = 0.5\text{pF}$$


Substituting these in eqns. for  $t_r$ ,  $t_f$ ,  $t_{dr}$  &  $t_{df}$  we get,

$t_r = 1.04\text{ns}$ , compared with  $1.14\text{ns}$  from SPICE (level 1)

$t_f = 0.83\text{ns}$ , compared with  $0.89\text{ns}$  from SPICE (level 1)

$t_{df} = 0.5\text{ns}$ , compared with  $0.52\text{ns}$  from SPICE (level 1)

 $t_{dr} = 0.4\text{ns}$ , compared with  $0.45\text{ns}$  from SPICE (level 1)





# Empirical Delay Models

- In an empirical delay model, a circuit simulator is used to model the inverter or gate in question and then the measured values are back substituted into appropriate delay equations

**Ex.:** One can back substitute into below equations to obtain values for  $A_N$  and  $A_P$ .

$$t_{df} = A_N \frac{C_L}{\beta_n} \quad \text{and} \quad t_{dr} = A_P \frac{C_L}{\beta_p}$$

$$A_P = t_{dr-spice} \frac{\beta_p}{C_L} = .52 \times 10^{-9} \times \frac{3.48 \times 10^{-4}}{0.5 \times 10^{-12}} = .36 \text{ (.31 calc)}$$

$$A_N = t_{df-spice} \frac{\beta_n}{C_L} = .45 \times 10^{-9} \times \frac{4.04 \times 10^{-4}}{0.5 \times 10^{-12}} = .36 \text{ (.29 calc).}$$


These constants may now be used to predict delay values for a wide range of gates. That is, for gates with  $W_p = 2W_n$ ,

$$t_{dr} = .36 \frac{C_L}{\beta_p} \qquad t_{df} = .36 \frac{C_L}{\beta_n}.$$

- Notice that these equations now represent the delay in terms of an RC delay where the effective resistance of the transistor is given by  $0.36/\beta$
 
# Gate Delays

- The delay of simple gates may be approximated by constructing an “equivalent” inverter.
- **Ex:** 3-input NAND gate



$$\beta_{neff} = \frac{1}{\frac{1}{\beta_{n1}} + \frac{1}{\beta_{n2}} + \frac{1}{\beta_{n3}}} \quad (\text{summation of series conductances}) \quad (4.51)$$

For  $\beta_{n1} = \beta_{n2} = \beta_{n3}$

$$\beta_{neff} = \frac{\beta_n}{3}.$$

For the pull-up case, only one p-transistor has to turn on to raise the output.  
Thus,

$$\beta_{peff} = \beta_p.$$

For  $\beta_p = 0.3 \beta_n$

$$t_r = k \frac{C_L}{0.3 \beta_n V_{DD}}, t_f = k \frac{C_L}{\frac{\beta_n}{3} V_{DD}}$$


$$\frac{t_r}{t_f} \approx 1.$$

For a more graphical understanding of this,

$$\beta_{\text{series}} = \beta_n / 3$$

Hence,

 
$$\tau_{\text{series}} = k \frac{C_L}{\frac{\beta_n}{3} V_{DD}}$$


 
# Switch-Level RC Models

RC modeling techniques represent transistors as a resistance discharging or charging a capacitance.

- Simple RC Delay Model
- Penfield-Rubenstein Delay Model
- Penfield-Rubenstein Slope Delay Model



# Simple RC Delay Model

# Penfield-Rubenstein Delay Model



# Penfield-Rubenstein Slope Model