

## Q & A

- IF THE WIDTH OF A TRANSISTOR INCREASES, THE CURRENT WILL  
**INCREASE** DECREASE NOT CHANGE
- IF THE LENGTH OF A TRANSISTOR INCREASES, THE CURRENT WILL  
INCREASE **DECREASE** NOT CHANGE
- IF THE SUPPLY VOLTAGE OF A CHIP INCREASES, THE MAXIMUM TRANSISTOR CURRENT WILL  
**INCREASE** DECREASE NOT CHANGE
- IF THE WIDTH OF A TRANSISTOR INCREASES, ITS GATE CAPACITANCE WILL  
**INCREASE** DECREASE NOT CHANGE
- IF THE LENGTH OF A TRANSISTOR DECREASES, ITS GATE CAPACITANCE WILL  
INCREASE **DECREASE** NOT CHANGE
- IF THE SUPPLY VOLTAGE OF A CHIP INCREASES, THE GATE CAPACITANCE OF EACH TRANSISTOR WILL  
INCREASE DECREASE **NOT CHANGE**

## Q & A

- IF THE WIDTH OF A TRANSISTOR INCREASES, THE CURRENT WILL  
INCREASE DECREASE NOT CHANGE
- IF THE LENGTH OF A TRANSISTOR INCREASES, THE CURRENT WILL  
INCREASE DECREASE NOT CHANGE
- IF THE SUPPLY VOLTAGE OF A CHIP INCREASES, THE MAXIMUM TRANSISTOR CURRENT WILL  
INCREASE DECREASE NOT CHANGE
- IF THE WIDTH OF A TRANSISTOR INCREASES, ITS GATE CAPACITANCE WILL  
INCREASE DECREASE NOT CHANGE
- IF THE LENGTH OF A TRANSISTOR DECREASES, ITS GATE CAPACITANCE WILL  
INCREASE DECREASE NOT CHANGE
- IF THE SUPPLY VOLTAGE OF A CHIP INCREASES, THE GATE CAPACITANCE OF EACH TRANSISTOR WILL  
INCREASE DECREASE NOT CHANGE




# CMOS INVERTER DESIGN


- Prashanth Kumar Shetty  
MSIS, Manipal
 
# CMOS INVERTER

CMOS inverter makes use of both NMOS and PMOS transistors



NMOS

 


PMOS

# OUTLINE


- ROBUSTNESS OF CMOS INVERTER – THE STATIC BEHAVIOR
  - SWITCHING THRESHOLD
  - NOISE MARGINS
- PERFORMANCE OF CMOS INVERTER – DYNAMIC BEHAVIOR
  - PROPAGATION DELAY
- POWER DISSIPATION
  - STATIC DISSIPATION
  - DYNAMIC DISSIPATION

# CMOS CIRCUITS

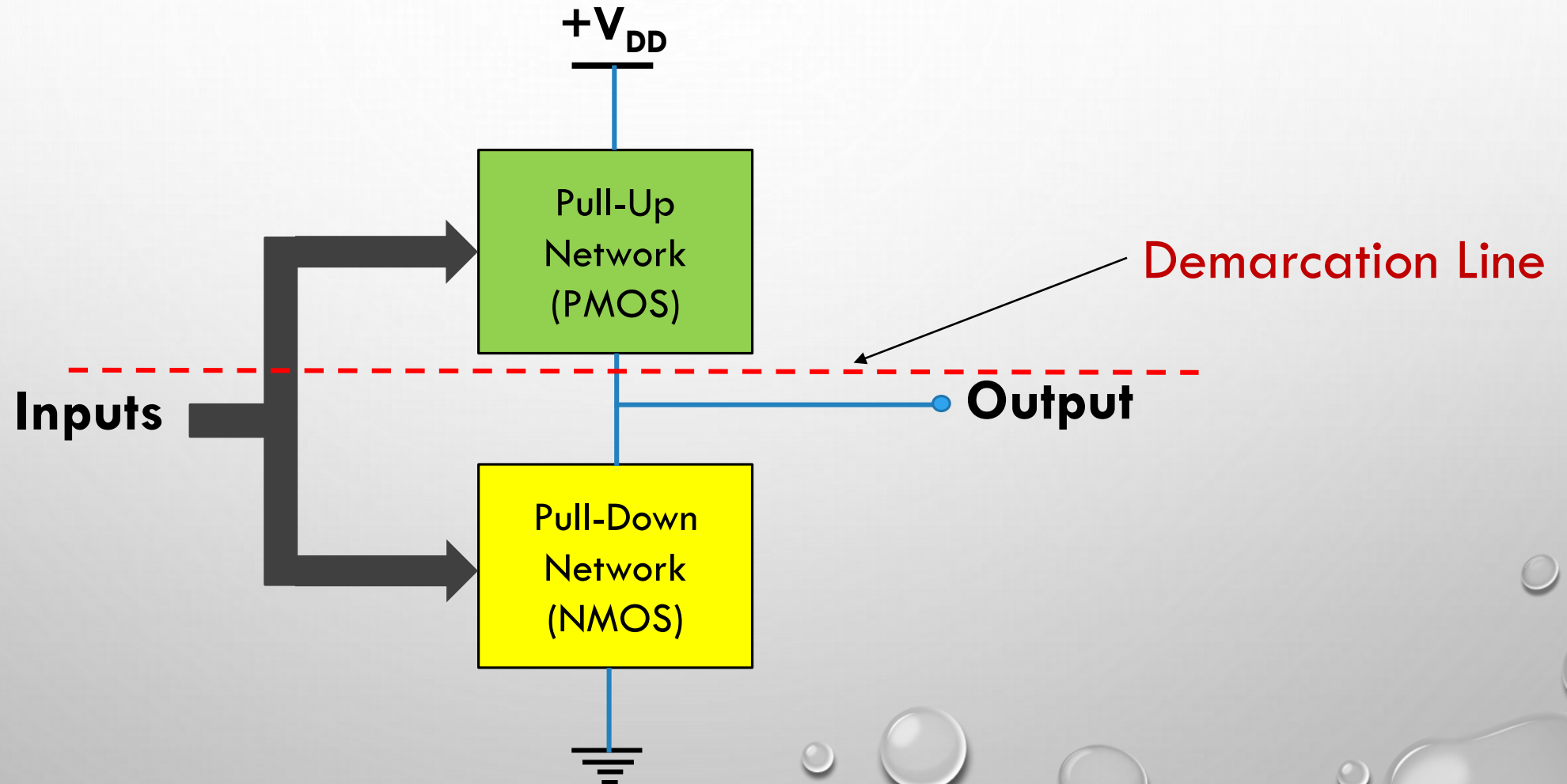



# CMOS INVERTER CIRCUIT

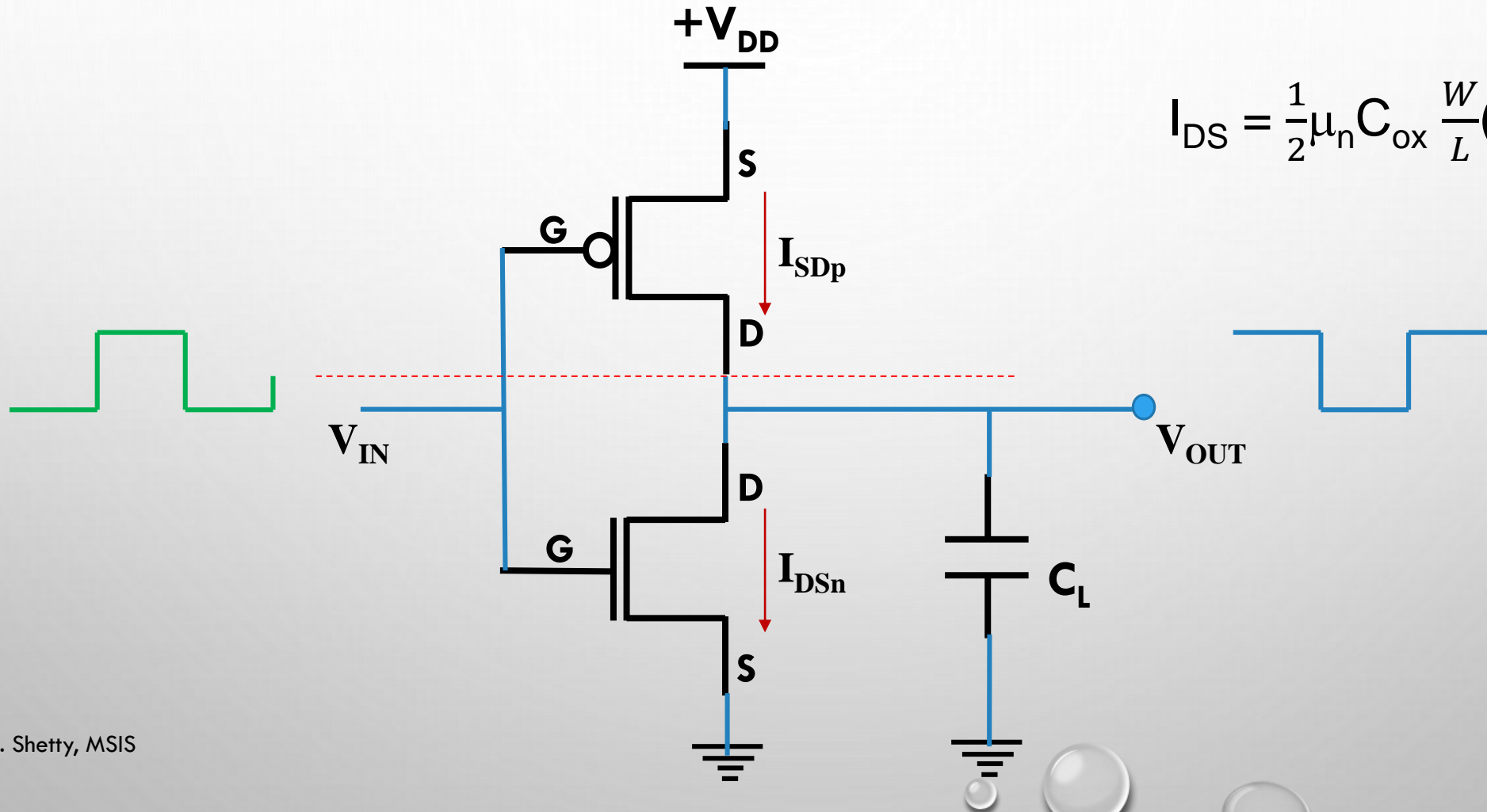

$$I_{DS} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

# Choosing the P and N Transistor Sizes

Two principal objectives: *Drive strength, Speed, Power, Noise margin*

- *To balance rise and fall drive strengths*  $\Rightarrow$  Conductances should be made equal

$$\mu_n \approx K \mu_p \quad \text{where } K = 2.7$$

$$\therefore W_p = K W_n$$

- *To make the gate as fast as possible*

Theoretically, the P to N transistor ratio which gives the fastest delay is  $K^{0.5}$


For an inverter, if  $K=2.7$ , this means a P:N transistor ratio of about **1.6**

**For inverters, a ratio of P=2N is commonly chosen as a compromise between fastest speed and balanced outputs.**



# CMOS INVERTER: DC ANALYSIS

- DC RESPONSE:  $V_{OUT}$  VS.  $V_{IN}$  FOR A GATE
- INVERTER
  - WHEN  $V_{IN} = 0 \rightarrow V_{OUT} = V_{DD}$
  - WHEN  $V_{IN} = V_{DD} \rightarrow V_{OUT} = 0$
  - IN BETWEEN,  $V_{OUT}$  DEPENDS ON TRANSISTOR CURRENT
  - BY KCL, MUST SETTLE SUCH THAT:  $I_{DSN} = |I_{DSP}|$
  - WE CAN SOLVE EQUATIONS
  - GRAPHICAL SOLUTION GIVES VERY GOOD INSIGHT

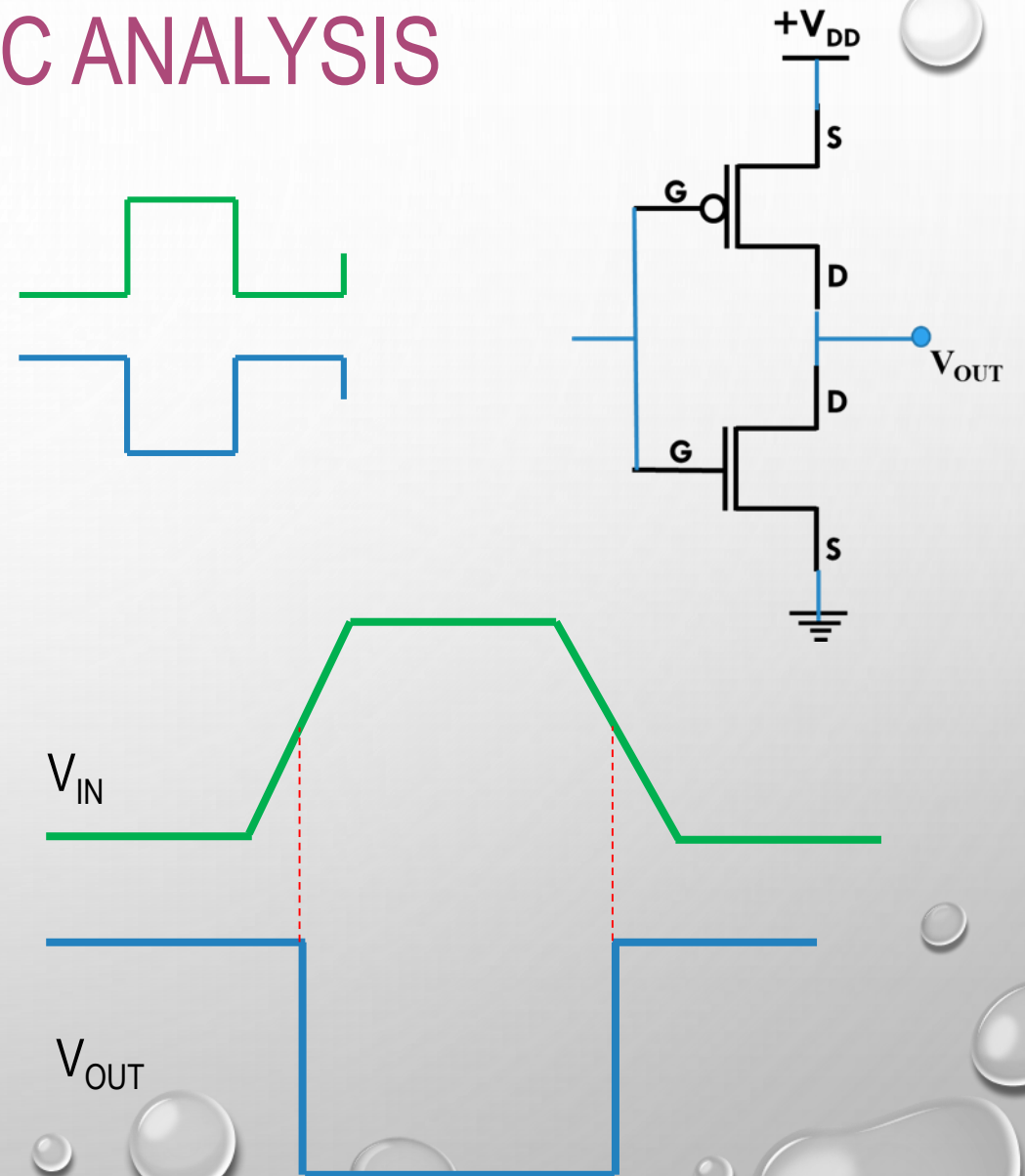

# TRANSISTORS OPERATION REGIONS

- CURRENT DEPENDS ON TRANSISTOR'S OPERATION REGION
- FOR WHAT  $V_{IN}$  AND  $V_{OUT}$  ARE NMOS AND PMOS IN
  - CUTOFF ?
  - LINEAR ?
  - SATURATION ?

# NMOS AND PMOS OPERATION

$$V_{GSN} = V_{IN}$$

$$V_{DSN} = V_{OUT}$$


$$V_{GSP} = V_{IN} - V_{DD}$$

$$V_{DSP} = V_{OUT} - V_{DD}$$

## Relationships between voltages for the three regions of operation of a CMOS inverter


	Cutoff	Linear	Saturated
nMOS	$V_{gsn} < V_{tn}$	$V_{gsn} > V_{tn}$	$V_{gsn} > V_{tn}$
	$V_{in} < V_{tn}$	$V_{in} > V_{tn}$	$V_{in} > V_{tn}$
		$V_{dsn} < V_{gsn} - V_{tn}$	$V_{dsn} > V_{gsn} - V_{tn}$
		$V_{out} < V_{in} - V_{tn}$	$V_{out} > V_{in} - V_{tn}$
pMOS	$V_{gsp} > V_{tp}$	$V_{gsp} < V_{tp}$	$V_{gsp} < V_{tp}$
	$V_{in} > V_{tp} + V_{DD}$	$V_{in} < V_{tp} + V_{DD}$	$V_{in} < V_{tp} + V_{DD}$
		$V_{dsp} > V_{gsp} - V_{tp}$	$V_{dsp} < V_{gsp} - V_{tp}$
		$V_{out} > V_{in} - V_{tp}$	$V_{out} < V_{in} - V_{tp}$

P.K. Shetty, MSIS

 
 
# GRAPHICAL DERIVATION OF THE INVERTER DC RESPONSE: I-V CHARACTERISTICS

- MAKE PMOS WIDER THAN NMOS SUCH THAT  $B_N = B_P$
- FOR SIMPLICITY LET'S ASSUME  $V_{TN} = -V_{TP}$





# GRAPHICAL DERIVATION OF THE INVERTER DC RESPONSE:

$I_{DS}$  vs.  $V_{out}$ ,  $V_{in}$

## • LOAD LINE ANALYSIS:

FOR A GIVEN  $V_{IN}$ :



- PLOT  $I_{DSN}$ ,  $I_{DSP}$  VS.  $V_{OUT}$
- $V_{OUT}$  MUST BE WHERE |CURRENTS| ARE EQUAL

  





# GRAPHICAL DERIVATION OF THE INVERTER DC RESPONSE: LOAD LINE ANALYSIS

- $V_{IN} = 0$

 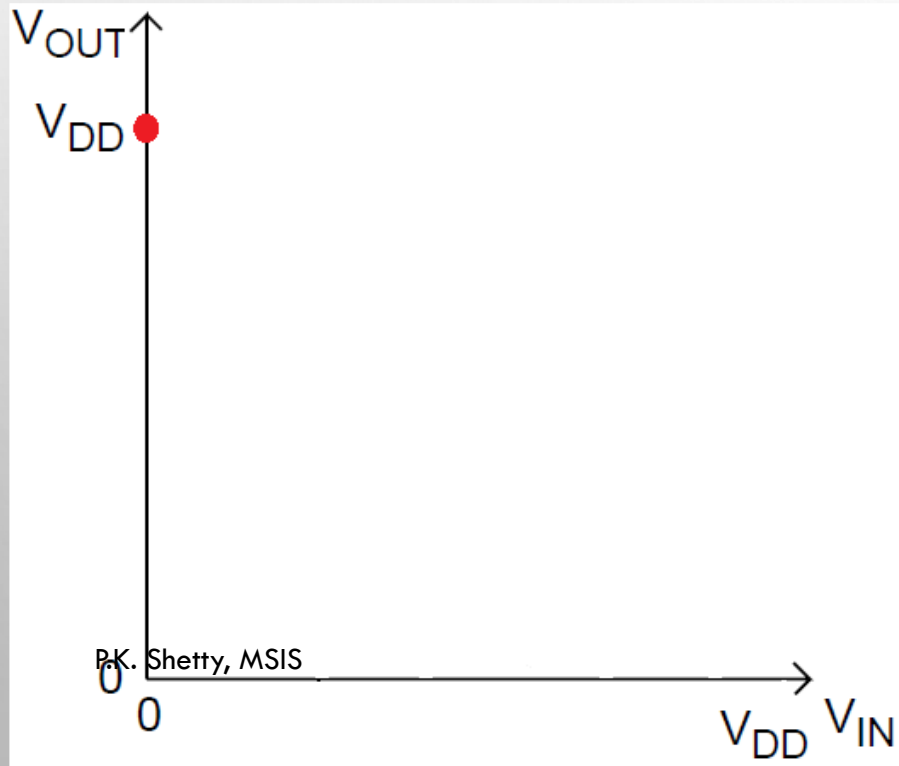



# GRAPHICAL DERIVATION OF THE INVERTER DC RESPONSE: LOAD LINE ANALYSIS

- $V_{IN} = 0.2V_{DD}$

  



# GRAPHICAL DERIVATION OF THE INVERTER DC RESPONSE: LOAD LINE ANALYSIS

- $V_{IN} = 0.4V_{DD}$

  



# GRAPHICAL DERIVATION OF THE INVERTER DC RESPONSE: LOAD LINE ANALYSIS

- $V_{IN} = 0.6V_{DD}$

 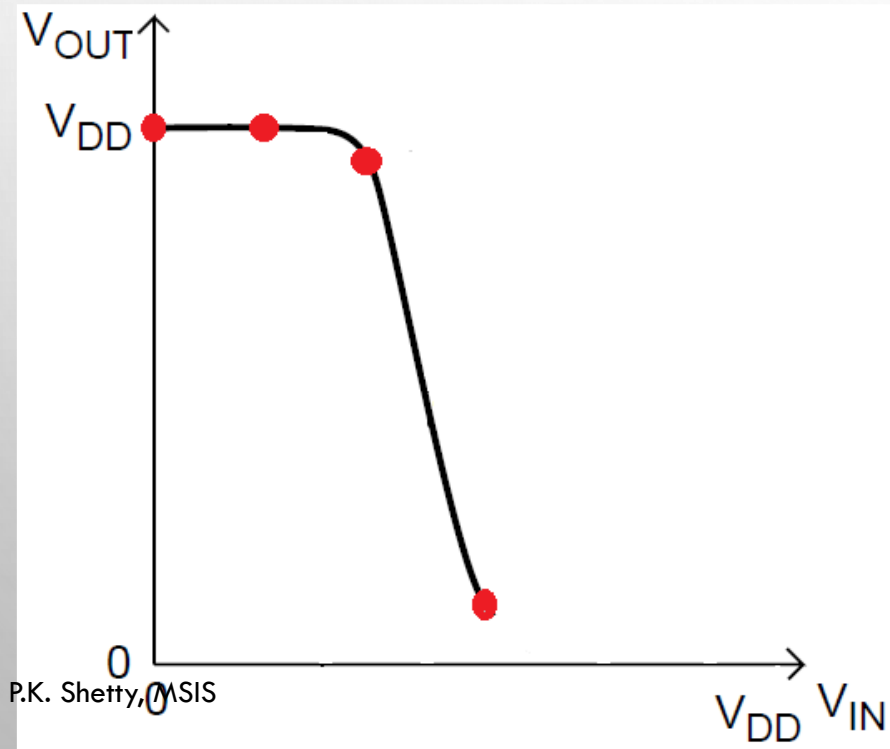

# GRAPHICAL DERIVATION OF THE INVERTER DC RESPONSE: LOAD LINE ANALYSIS



- $V_{IN} = 0.8V_{DD}$

 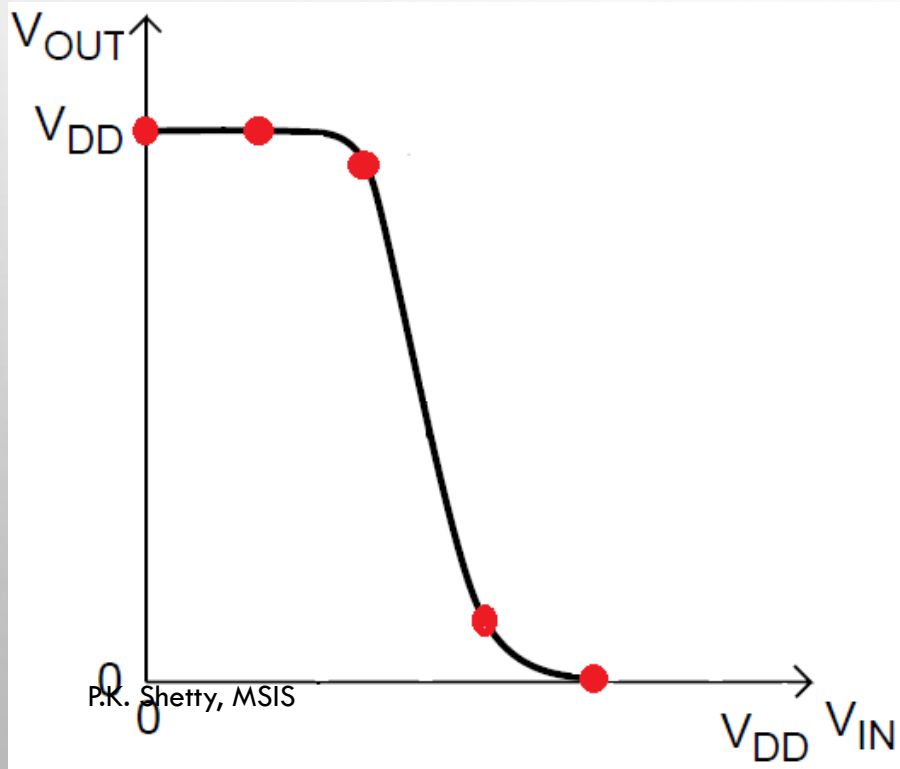




# GRAPHICAL DERIVATION OF THE INVERTER DC RESPONSE: LOAD LINE ANALYSIS

- $V_{IN} = V_{DD}$

 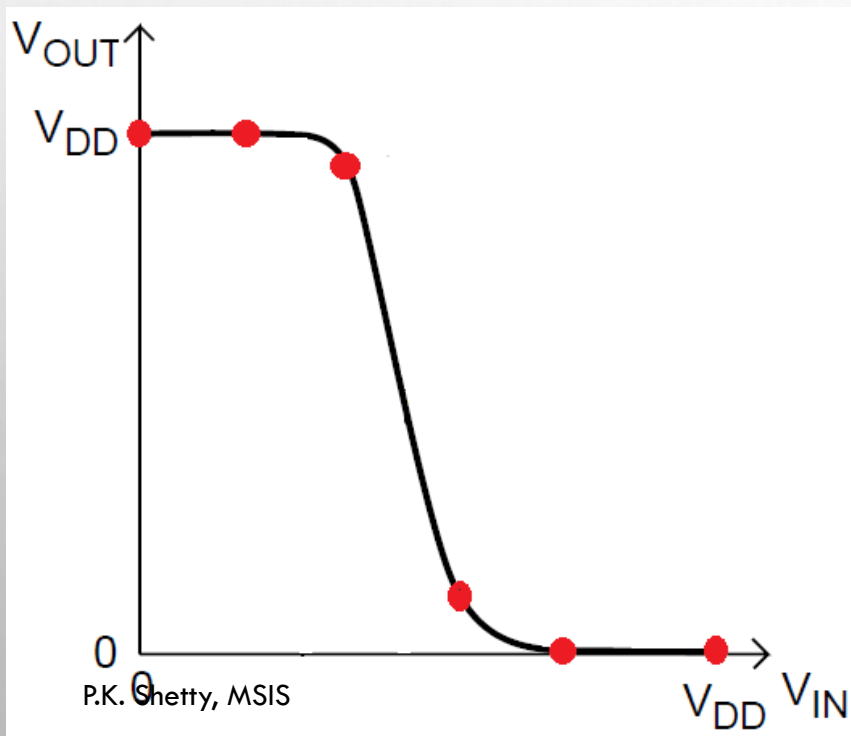

 
# DC TRANSFER CURVE

- TRANSCRIBE POINTS ONTO  $V_{IN}$  VS.  $V_{OUT}$  PLOT




In region C both transistors are in saturation.  
 Ideal transistors are only in region C for  $V_{in} = \frac{V_{DD}}{2}$   
 and the DC curve slope in C is  $-\infty$ .

 The crossover point where  $V_{in} = V_{out}$  is called input threshold.





Relationships between voltages for the three regions of operation of a CMOS inverter			
	Cutoff	Linear	Saturated
nMOS	$V_{gsn} < V_{tn}$	$V_{gsn} > V_{tn}$	$V_{gsn} > V_{tn}$
	$V_{in} < V_{tn}$	$V_{in} > V_{tn}$	$V_{in} > V_{tn}$
		$V_{dsn} < V_{gsn} - V_{tn}$	$V_{dsn} > V_{gsn} - V_{tn}$
		$V_{out} < V_{in} - V_{tn}$	$V_{out} > V_{in} - V_{tn}$
pMOS	$V_{gsp} > V_{tp}$	$V_{gsp} < V_{tp}$	$V_{gsp} < V_{tp}$
	$V_{in} > V_{tp} + V_{DD}$	$V_{in} < V_{tp} + V_{DD}$	$V_{in} < V_{tp} + V_{DD}$
		$V_{dsp} > V_{gsp} - V_{tp}$	$V_{dsp} < V_{gsp} - V_{tp}$
		$V_{out} > V_{in} - V_{tp}$	$V_{out} < V_{in} - V_{tp}$

 


Summary of CMOS inverter operation				
Region	Condition	p-device	n-device	Output
A	$0 \leq V_{in} < V_{tn}$	linear	cutoff	$V_{out} = V_{DD}$
B	$V_{tn} \leq V_{in} < V_{DD}/2$	linear	saturated	$V_{out} > V_{DD}/2$
C	$V_{in} = V_{DD}/2$	saturated	saturated	$V_{out}$ drops sharply
D	$V_{DD}/2 < V_{in} \leq V_{DD} -  V_{tp} $	saturated	linear	$V_{out} < V_{DD}/2$
E	$V_{in} > V_{DD} -  V_{tp} $	cutoff	linear	$V_{out} = 0$

# DC TRANSFER CURVE: OPERATING REGIONS

  


A CMOS inverter

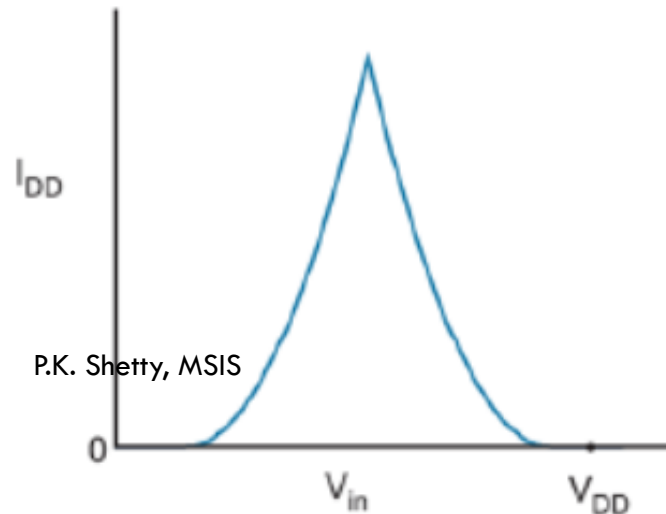

P.K. Shetty, MSIS

Summary of CMOS inverter operation				
Region	Condition	p-device	n-device	Output
A	$0 \leq V_{in} < V_{tn}$	linear	cutoff	$V_{out} = V_{DD}$
B	$V_{tn} \leq V_{in} < V_{DD}/2$	linear	saturated	$V_{out} > V_{DD}/2$
C	$V_{in} = V_{DD}/2$	saturated	saturated	$V_{out}$ drops sharply
D	$V_{DD}/2 < V_{in} \leq V_{DD} -  V_{tp} $	saturated	linear	$V_{out} < V_{DD}/2$
E	$V_{in} > V_{DD} -  V_{tp} $	cutoff	linear	$V_{out} = 0$

# Inverter Voltage Transfer Curve

 



 
# Inverter Threshold, $V_{INV}$

In Region C, both the transistors are in saturation region. That is equivalent to two current sources in series which is an unstable condition.

$$V_{in} = \frac{V_{DD} + V_{tp} + V_{tn} \sqrt{\frac{\beta_n}{\beta_p}}}{1 + \sqrt{\frac{\beta_n}{\beta_p}}}$$




In this point,  $V_{in} = V_{out}$  and actual state transition takes place at this point. Hence this is also called as Inverter Threshold,  $V_{inv}$ .


If  $V_{tn} = V_{tp}$  and  $\beta_n = \beta_p$ , then,  $V_{in} = V_{DD}/2 \Rightarrow$  Good noise margin
 
## $V_{inv}$ vs. $\beta_n/\beta_p$


- If  $\beta_p/\beta_n \neq 1$ , switching point will move from  $V_{DD}/2 \Rightarrow$  skewed gate
- If  $\beta_p > \beta_n \Rightarrow$  High skewed inverter
- If  $\beta_p < \beta_n \Rightarrow$  Low skewed inverter



P.K. Shetty, MSIS

 

# Simulation using Cadence Virtuoso

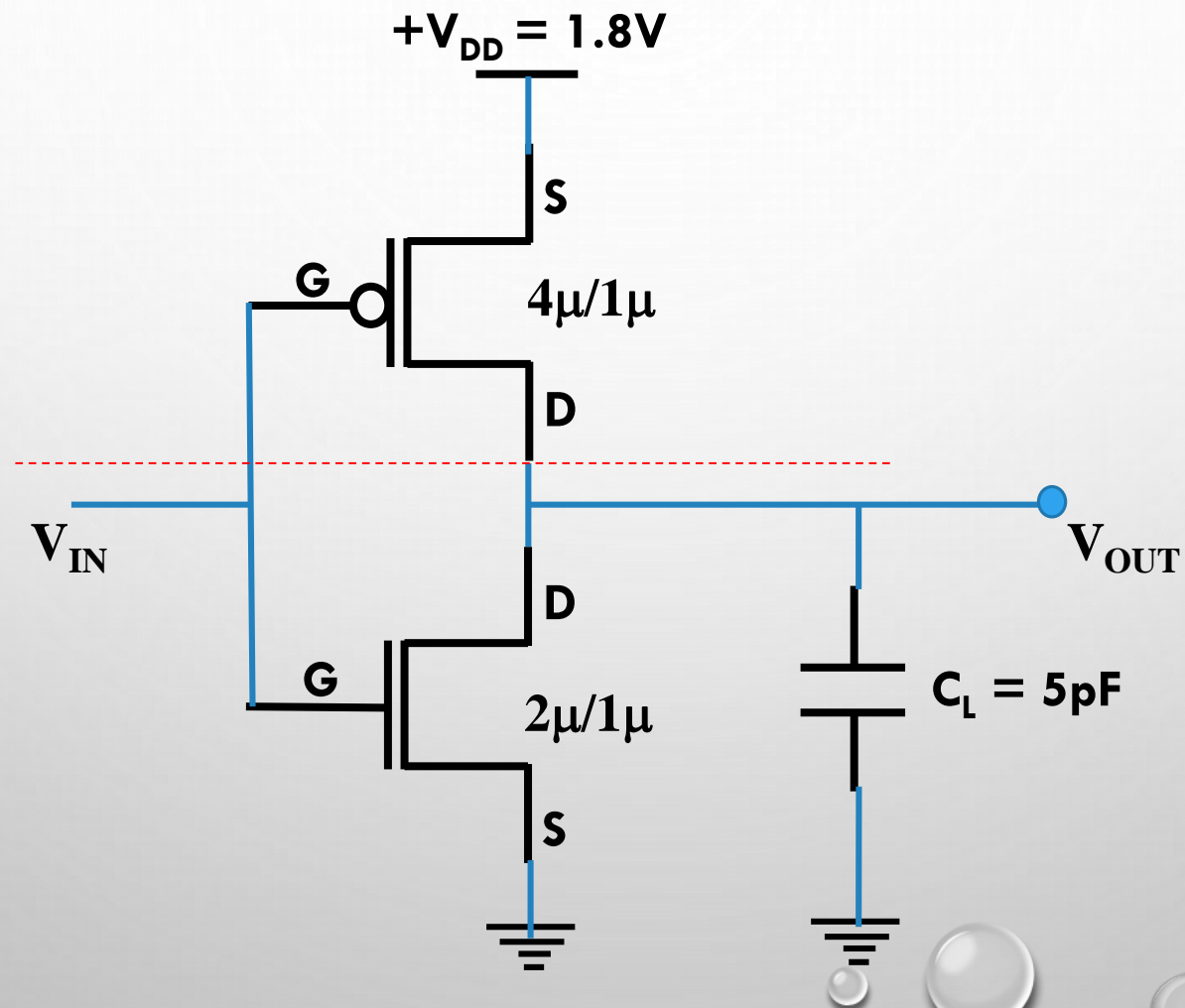


# NOISE MARGIN

## Noise margin


- is the amount of noise that a CMOS circuit could withstand without compromising the operation of circuit
- does make sure that any signal which is logic '1' with finite noise added to it, is still recognized as logic '1' & not logic '0'
- is a parameter closely related to the input-output voltage characteristics
- allows us to determine the allowable noise voltage on the input of a gate so that the output will not be affected

# NOISE MARGIN

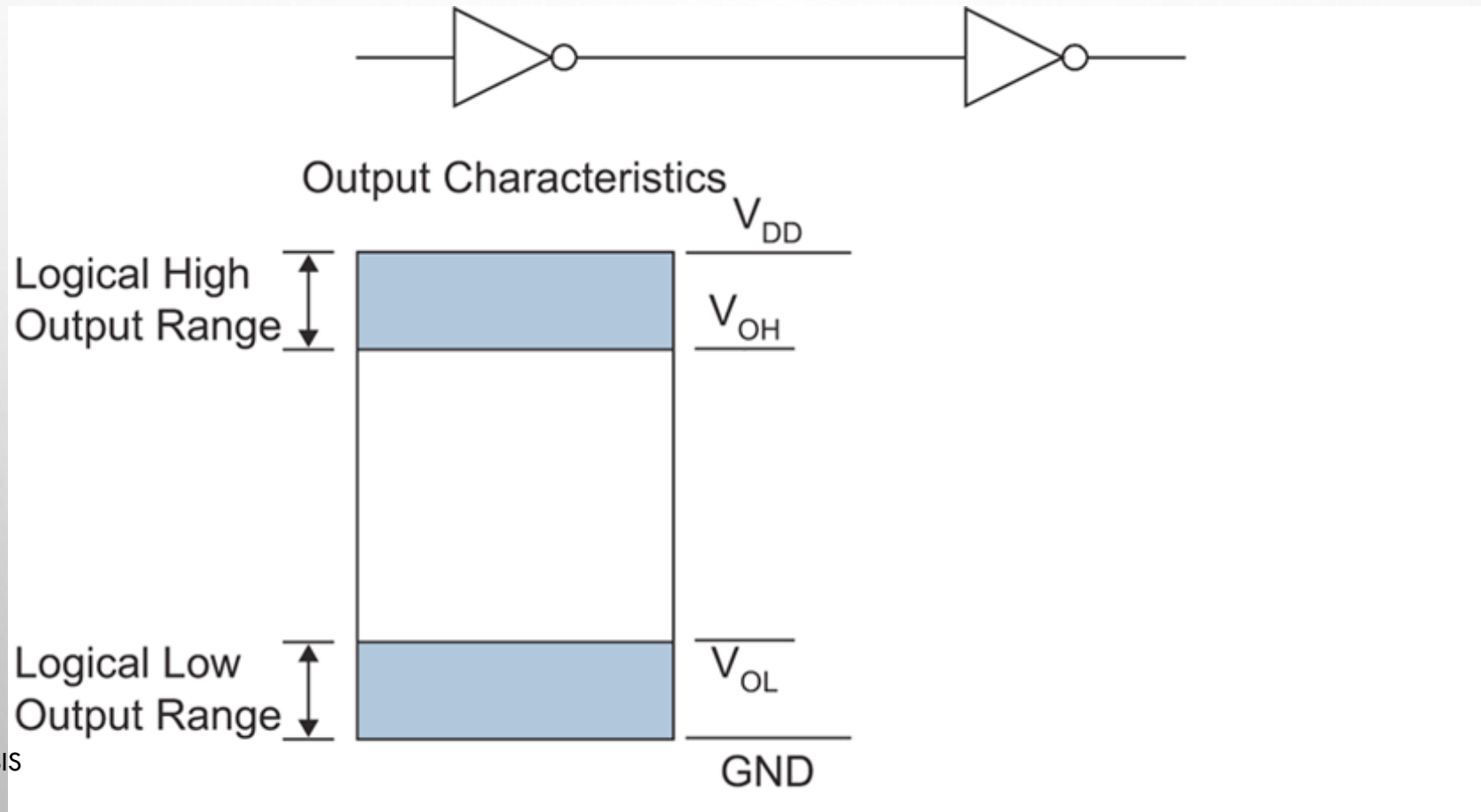




# NOISE MARGIN

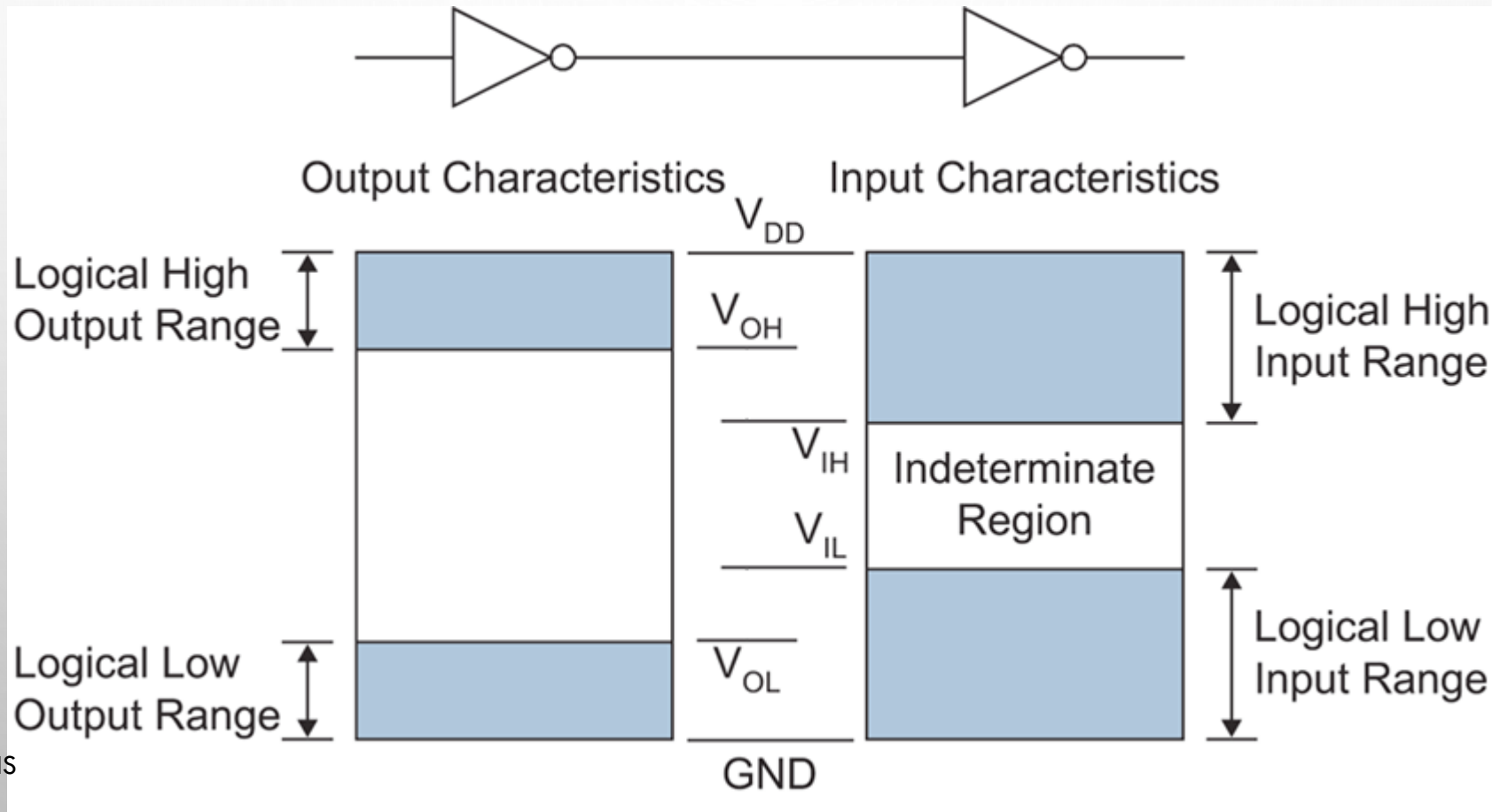

# NOISE MARGIN

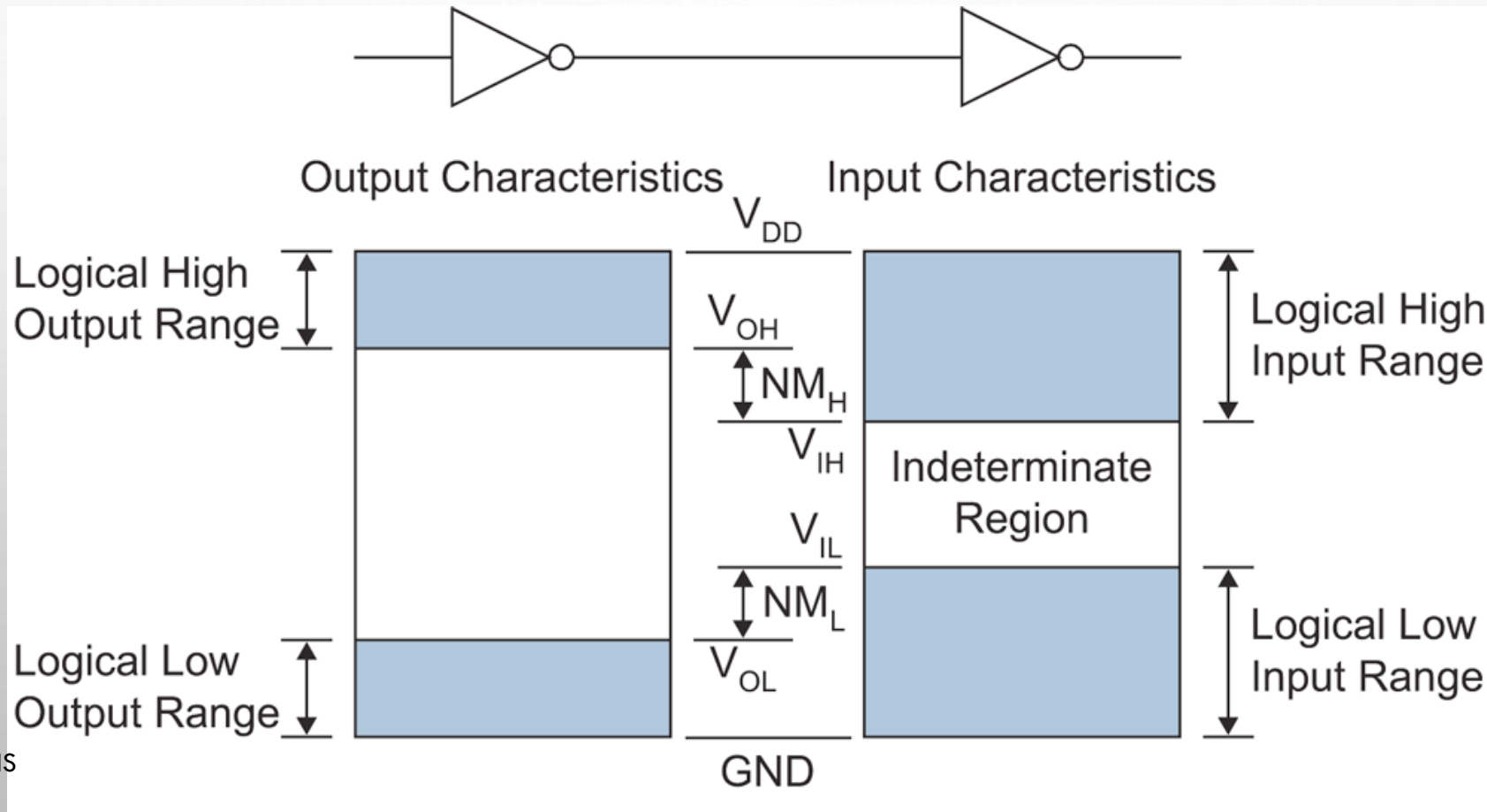

# NOISE MARGIN

- Noise margin is specified in terms of 2 parameters:
  - LOW Noise Margin,  $NM_L$
  - HIGH Noise Margin,  $NM_H$

$$NM_L = |V_{ILmax} - V_{OLmax}|$$

$$NM_H = |V_{OHmin} - V_{IHmin}|$$

To optimize both noise margins  $NM_L$  and  $NM_H$  generally it is desirable to have  $V_{IH} = V_{IL}$  & this to be a value that is midway in the logic swing, that is  $V_{DD}/2$ .

$$\text{Or, } V_{inv,th} = V_{DD}/2$$


# NOISE MARGIN

- To maximize noise margins, select logic levels at unity gain point of DC transfer char.


For our Inverter,

$$NM_L = |V_{ILmax} - 0V|$$

$$NM_H = |V_{DD} - V_{IHmin}|$$

 

# Noise Margin Calculation

 

- Calculate  $V_{INV}$
- Calculate  $A_V(V_{INV})$
- Calculate  $NM_L$  and  $NM_H$


# Calculate $V_{INV}$

$$V_{INV} = \frac{V_{DD} + V_{tp} + V_{tn} \sqrt{\frac{\beta_n}{\beta_p}}}{1 + \sqrt{\frac{\beta_n}{\beta_p}}}$$



If  $V_{tn} = -V_{tp}$  and  $\beta_n = \beta_p$ , then,  $V_{INV} = V_{DD}/2$



# Calculate $A_v$ ( $V_{INV}$ )

 

Small Signal Model

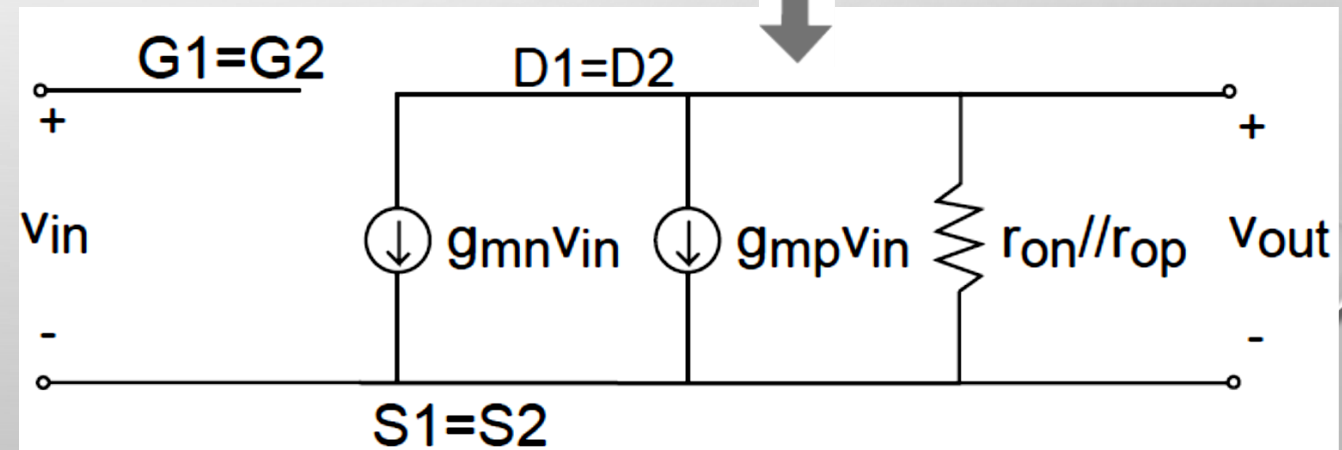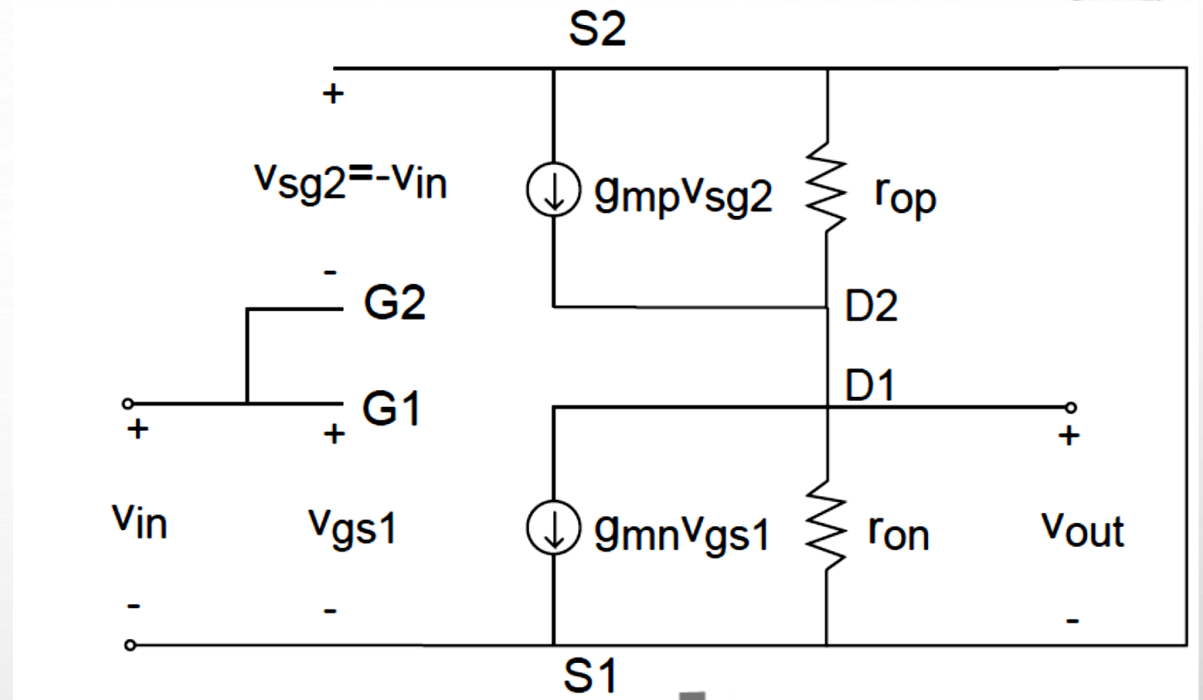

$$A_v = -(g_{mn} + g_{mp})(r_{on} // r_{op})$$

P.K. Shetty, MSIS

# Noise Margin Calculation

- Noise-margin low,  $NM_L$ :

$$V_{IL} = V_{INV} - \frac{V_{DD} - V_{INV}}{|A_v|}$$

$$NM_L = V_{IL} - V_{OL} = V_{IL} = V_{INV} - \frac{V_{DD} - V_{INV}}{|A_v|}$$

- Noise-margin high,  $NM_H$ :

$$V_{IH} = V_{INV} \left( 1 + \frac{1}{|A_v|} \right)$$

$$NM_H = V_{OH} - V_{IH} = V_{DD} - V_{INV} \left( 1 + \frac{1}{|A_v|} \right)$$


# STANDARD SIMPLE GATES

CMOS schematics of:

- NOR Gate
- NAND Gate


## 2- INPUT NOR GATE

$$F = \overline{A + B}$$

 

## 2- INPUT NAND GATE

$$F = \overline{A \cdot B}$$

 


# COMPOUND CMOS GATES

Design CMOS logic gates for the following functions:


1.  $F = (A.B + C.D)'$
2.  $F = ((A+B+C).D)'$
3.  $Z = (((A.B) + C).D)'$
4.  $Z = ((A.B) + C.(A+B))'$




$$F = \overline{(A.B + C.D)}$$

 


$$F = \overline{(A.B + C.D)}$$

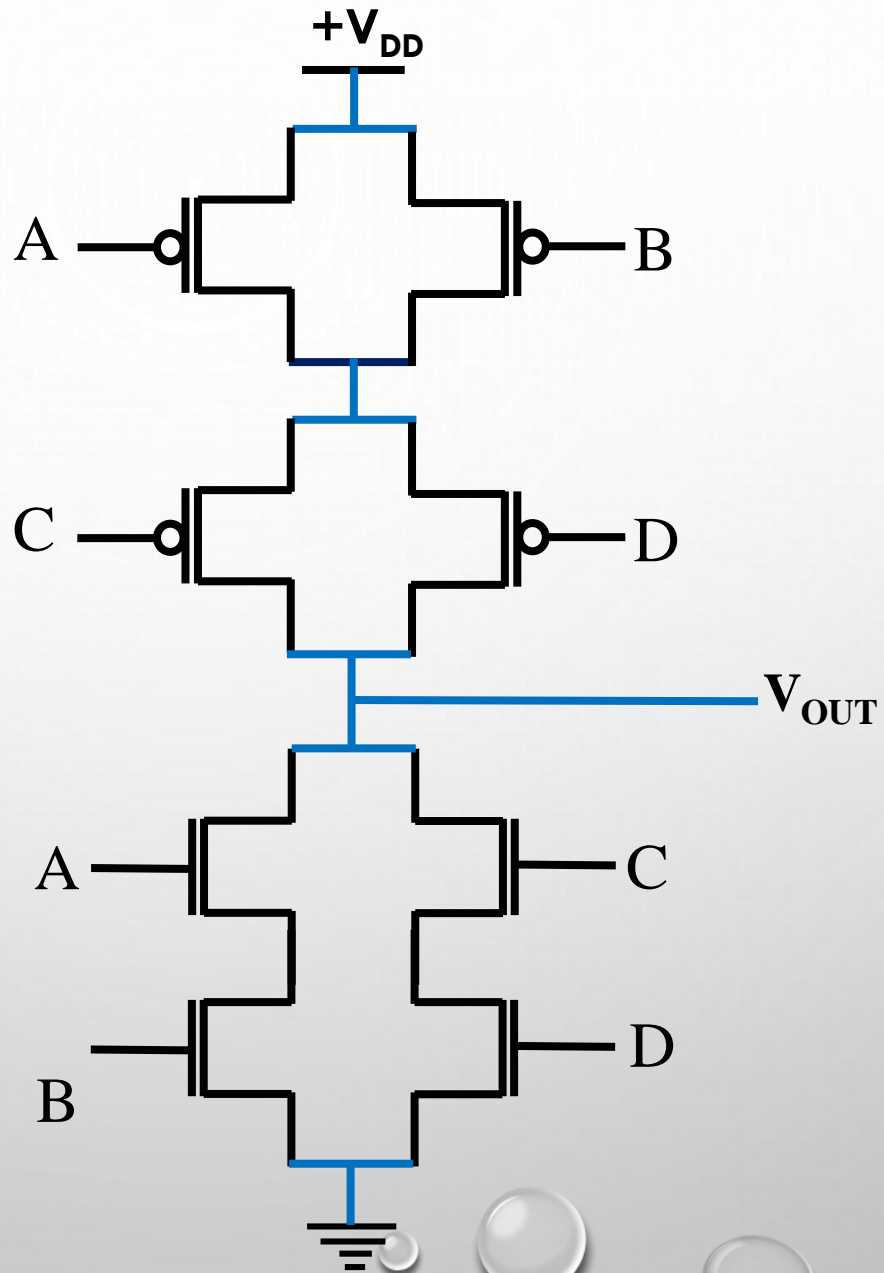

 

$$F = \overline{(A+B+C)}.D$$

 

# COMPOUND CMOS GATES

- Can a compound gate be arbitrarily complex?
  - NO, propagation delay is a strong function of fan-in:

$$t_p = a_0 \cdot FO + a_1 \cdot FI + a_2 \cdot (FI)^2$$

- FO  $\Rightarrow$  Fan-out, number of loads connected to the gate:
  - 2 gate capacitances per FO + interconnect
- FI  $\Rightarrow$  Fan-in, Number of inputs in the gate:
  - Quadratic dependency on FI due to:
    - Resistance increase
    - Capacitance increase
- Avoid large FI gates (Typically  $FI \leq 4$ )

